



amateur radio

Vol. 34, No. 2
FEBRUARY
1966

Registered at G.P.O., Melbourne, for
transmission by post as a periodical

25c

MICROPHONES

CRYSTAL:
Piezo Lapel Type with Plug 12/6
C250 Hand Type with Plug 21/6
X43 Stand Type with Plug 37/6
BM3 Pencil Type 100-5,000 c/s. with on-off switch, 6 ft. cable 21/6
BM3 Desk Stand to suit above 21/-

DYNAMIC:
Foster DP2 Hand Type 20K 58/6
Foster DP2 Hand Type 30 ohm 45/-
Foster DP2 Pencil Type 20K 90/-
Foster DP2 Pencil Type 30 ohm 87/6
Foster X20 Desk Type with stand, low impedance 87/6

GRID DIP OSCILLATORS

Lafayette TE-15 G.D.O., 4 Bands, Plug in Coils, 200 Kc.-250 Mc., 243 volt £19/15/-
Leader LDM-810 G.D.O., 2-250 Mc., 6 Band, Plug-in Coils, 230 volt £22/15/-

CHASSIS PUNCH SET

Hozan K-33 Sizes 15, 18, 21, 25 and 30 mm., complete with Taper Reamer in wooden storage box 70/-

TAPERED REAMERS

Hozan Tapered Reamer, 3 mm., 14 mm. 11/-

SAKURA CIRCUIT TESTER

Model TR53
Sensitivity: d.c. 20,000 ohms/volt, a.c. 10,000 ohms/volt. Voltages: 0, 10, 20, 100, 200, 1,200; a.c. voltages: 6, 30, 120, 600, 1,200. D.C. current, 60 μ A, 6 mA, 60 mA, 600 mA. Resistance: 10K, 100K, 1M, 10M ohms. Capacitance: 0.001-0.2 μ F, 0.0001-0.01 μ F. Inductance: 30-3,000H. Decibels: minus 20 to plus 17 db. 10 db. -5.75V. 60 ohm. Dimensions: 4 1/4 x 6 1/4 x 2 1/4 in. Weight 1.5 lbs.

Price £8/10/0

COAXIAL CABLES

UR57 50 ohm 3/4 in. diam. coaxial cable, 1/6 yd. or 25/- per 25 yds. roll, 10/- postage.
UR43 50 ohm 3/16 in. diam. coaxial cable 15/- per 25 ft. roll, 10/- postage.
UR31 72 ohm 1/4 in. diam. coaxial cable, 1/6 yd. or 1/- per 25 yds. roll.
51 ohm RG-10 1/4 in. diam., brand new. 1/6 yd. up to 500 yard lengths.
All above cables are in as new condition.

BATTERY CHARGERS

DUAL COMPLETE WITH METER IN METAL HAMMERTON CASE
6 volt 4 amp, 12 volt 4 amp. £7/17/6.
12 volt 6 amp, 6 volt 6 amp. £7/17/6.

TRANSISTORISED AMPLIFIERS AND TUNERS

LAFAYETTE
PK-523 3 Transistor, single ended 50 mW. output £7/17/6
PK-543 4 Transistor, push pull, 100 mW. output £7/17/6
PK-544 4 Transistor, push pull, 250 mW. output £7/17/6
PK-501 4 Transistor, push pull, 1 watt output £7/17/6
PK-523 3 Transistor, 1 Diode, broadcast a.m. tuner £6/15/6


SPEAKER BOXES

Plastic Speaker Box with 4 in. Speaker and Wire 35/-
Wooden Speaker Box with 6 in. x 4 in. Speaker and Wire 65/-

LOG BOOKS 6/6 each, postage 1/-
CALL BOOKS, 6/- each, postage 1/-

MULTIMETER Model 200H

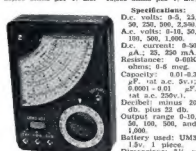20,000 ohms per v. d.c. 10,000 ohms per v. a.c.



Complete with internal battery, testing leads and probe.

Price £5/12/6 inc. tax.
Pecking and Postage 3/6

TRANSISTORS AND DIODES

OC44	16/-	OA79	1/6
OC45	16/-	OA80	3/6
OC46	15/6	OA81	3/6
OC71	7/6	3 at £1	3/6
OC72	16/-	OA210 1N1783	8/6
OC74	15/6	OA211 510A82	17/6
OC75	13/6	ZENER	17/6
OC170	16/-	OA224 BZ216	27/6
OC171	16/-	OA222 BZ214	27/6

ADEL NIBBLING TOOL

Designed to cut round or square holes in sheet metal, with instructions 13/-

HI FIRE TRANSISTORISED IGNITION SYSTEM

6 OR 12 VOLT

POSITIVE EARTH £2/6
NEGATIVE EARTH £2/6

RECORDING TAPES

WELL-KNOWN	MAKES	BRAND NEW	IN
150 ft. on 3 in. reel	(Acetate Base)	6/-	
225 ft. on 3 in. reel	(Acetate Base)	7/6	
300 ft. on 3 in. reel	(Tensilised Mylar)	10/-	
300 ft. on 3 in. reel	(Tensilised Mylar)	10/-	
600 ft. on 3 1/4 in. reel	(Tensilised Mylar)	17/6	
900 ft. on 5 in. reel	(Acetate Base)	19/6	
900 ft. on 5 in. reel	(Mylar Base)	22/6	
1200 ft. on 5 in. reel	(Mylar Base)	25/6	
1200 ft. on 5 1/4 in. reel	(Tensilised Mylar)	32/6	
1200 ft. on 5 1/4 in. reel	(Tensilised Mylar)	32/6	
1200 ft. on 7 in. reel	(Acetate Base)	35/-	
1200 ft. on 7 in. reel	(Mylar Base)	35/-	
1200 ft. on 7 in. reel	(Acetate Base)	35/-	
1200 ft. on 7 in. reel	(Mylar Base)	40/6	
2400 ft. on 7 in. reel	(Mylar Base)	39/6	
3600 ft. on 7 in. reel	(Tensilised Mylar)	75/-	
3600 ft. on 7 in. reel	(Tensilised Mylar)	95/6	

EMPTY TAPE REELS

3 in., 2 1/4, 3 1/4, 3 1/2, 4 in., 5 in., 5 1/2, 5 3/4, 6 in., 7 in., 8 in., 999 in., 1000 in.

OR IN Plastic Storage Box 12/-

TAPE SPLICERS Complete with Splicing Tape and instructions 3/-

SPECIALS

Sato Subminiature Bezel, 5-8 volt, No. 3230 complete with globe, Red or Black 4/-
RESIN CORE SOLDER, 16 gauge. 18/-
40-43, 1 lb. packet 22/-
50-48, 1 lb. packet 22/-
Mixed Bag of NEW Resistors, Condensers, Potentiometers, 30 Popular Types. £1 or 16/- a bag.
Mixed Bag of 20 NEW Polyester and Styrofoam Capacitors. All Popular Types. £1 or 16/- a bag.
Mixed Bag of 20 NEW Polyester, Paper, Mica Ceramic and Plastic Condensers. All Popular Types. £1 or 16/- a bag.
1 Henry choke for Mullard Tachometer 22/6
Crystal Ear piece for Transistor Radio 8/6
Crystal Lapel Microphone 15/6

WALKIE TALKIES

8 Transistor 100 mW. output Citizens Band, 27.245 Mc. Fully transistorised Walkie Talkies. Individual speaker and microphone. Dimensions: 7 1/4 x 2 1/4 x 2 in. Complete with batteries, earphone and leather carrying case. £39/10/0
Inc. tax, plus freight.

MULTIMETERS

CENTRAL CT350 Multimeter, 20,000 Ω /v. £2/10/6
CENTRAL CT350 Multimeter, 20,000 Ω /v. d.c. £4
SANSAL SE350 Multimeters, 100,000 Ω /v. £3/5/-
Multimeter Probes 6/-
250M Movement 37/6
Meter Rectifiers 16/-

SOLDERING IRONS

"SCOPE" 6-second Soldering Iron, recommended work, voltage: 4v, a.c. d.c. 1100v. 43/-
"SCOPE" de luxe model, as above, with stainless steel barrel, in plastic pouch 30/-
"MINISCOPE" Soldering Iron (user standard transformer), in plastic pouch 43/-
TRANSFORMER suitable for Scope or Birko Soldering Iron 52v. to 33v. 30/-
"BIRKO" 6-second Soldering Iron, 4 to 4v. a.c. d.c., in plastic pouch 20/6
Or with transformer £4/4/6

SPEAKERS

WELL KNOWN MAKE, BRAND NEW, BANKRUPT STOCK
2 in. 15 ohm 30/- 5 in. x 7 in. 15-35 47/6
3 in. 15-35 32/6 8 in. 15-35 52/6
4 in. 15-35 37/6 9 in. x 6 in. 15-35 53/-
5 in. 15-35 40/- 15 in. 15-35 82/6
6 in. 15-35 42/-

TWIN CONE SPEAKERS

3 in. Twin Cone 4w, 15 ohm 44/-
8 in. Twin Cone 15w, 15 ohm 77/6
12 in. Twin Cone 15w, 15 ohm 106/-

CORDOVER SOLID STATE MODULES

22 different types, S.S. amplifiers, electronic siren, burglar alarm, intercom, module, auto amplifier module, phonograph amplifier module, wireless microphone module, and many others. Dimensions: 1 1/2 x 3 1/2 x 1 inch.

Price approx. £4 per unit
Send stamped, addressed envelope for more details.

ROTARY SWITCHES

3 pole, 2 position, 18/-; 4 pole, 3 position, 18/-; 2 pole, 6 position, 18/-; 1 pole, 12 position, 18/-.

HAM RADIO SUPPLIES

5A MELVILLE STREET, HAWTHORN, VICTORIA Phone 86-6465

North Balwyn tram passes corner.

Money Orders and Postal Notes payable North Hawthorn P.O.

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, New Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc.

"AMATEUR RADIO"

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA FOUNDED 1910

FEBRUARY 1966

Vol. 34, No. 2

Editor:

K. M. COCKING VKJZFQ

Assistant Editor:

K. E. Pinnett VKJAFJ

Publications Committee:

G. W. Saly (Secretary) VKJAGM
A. W. Chandler (Circulation) VKJALC
S. T. Clark VKJASC
E. C. Manifold VKJEM
W. E. J. Roper VKJAEZ

Draughtsmen—

Ken Gillespie VKJGK
Clem Allen VKJIV
Ian Smith 36 Green St., Noble Park

Advertising Enquiries:

C/o P.O. Box 36, East Melbourne, C.S. Vic.
or
Mrs. BELLAIRS, Phone 41-3525, 479 Victoria
Parade, East Melbourne, C.S. Victoria. Hours
10 a.m. to 3 p.m. only.

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 55a Franklin St., Melbourne, Vic.

Printers:

"RICHMOND CHRONICLE" Phone 42-3418.
Shakespeare St., Richmond, E.I. Vic.

★

All matters pertaining to "A.R." other than subscriptions, should be addressed to:

THE EDITOR.

"AMATEUR RADIO,"

P.O. BOX 38,
EAST MELBOURNE, C.S. VIC.

Acknowledgments will be sent following the Committee meeting on the second Monday of each month. All Sub-Editors should forward their articles to reach "A.R." before the 8th of each month. Any item received after the Committee meeting will be held over until the next month. Publication of any item is dependent upon space availability, but in general about two months may elapse before a technical article is published after consideration by the Publications Committee.

★

Members of the W.I.A. should refer all enquiries regarding delivery of "A.R." direct to their Divisional Secretary and not to "A.R." direct. Non members of the W.I.A. should write to the Victorian Division, C/o P.O. Box 36, East Melbourne. Two months' notice is required before a change of mailing address can be effected. Readers should note that any change in the address of their transmitting station must, by P.M.G. regulation, be notified to the P.M.G. in the form of residence. In addition "A.R." should also be notified. A convenient form is provided in the "Call Book".

★

Direct subscription rate is 30/- a year, post paid, in advance. Issued monthly on the first of the month. January edition excepted.

FEDERAL COMMENT

★

43K . . . AND A SUGGESTION

This business of I.T.U. and associated matters may seem, to many Amateurs, a topic thrashed to death by this Institute. Whilst there have been many appeals made in the past for considered views on this all important question of Amateur frequencies, it is true to say that we have been rather narrow in our view of the situation, and little attempt has been made to find out what other Societies in our Region think, and in particular what are their most pressing problems when it comes to the question of frequencies, and operating conditions.

Region III. is made up of Amateurs from Burma, Ceylon, Hong Kong, India, Japan, and of course, Australia, with a total licensed Amateur population of some 43,000; not large as Amateur populations go in other parts of the globe, and when one considers that 38,000 are to be found in Japan, our own total is rather insignificant by comparison.

It is rather refreshing to find, therefore, that the Amateur Radio Society of India with 360 members have had sufficient inspiration to make a suggestion which can do nothing but good if we can follow it through.

Writing in the official Newsletter of the A.R.S.I., the Western Zone have proposed that "to safeguard Amateur frequencies we must establish an organisation of member societies of the I.A.R.U. in Region III. (similar to that which has operated so successfully since 1950 in Region I. (Europe and Africa). If this is done a regular exchange of views at executive level will become possible through the medium of Regional Conferences and Regional Committees."

We would like to be able to meet personally representatives from other member societies in this Region, and through discussion, find some common ground which, it is hoped, would reflect the aim which, basically, all Amateurs share. A united front in Region III, with one or more delegates from member countries demanding our rights at the next conference, must surely stand a chance of success. Perhaps all this is wishful thinking; but by no means is the situation overstated.

We realise that to do this money is required and apart from Australia and Japan what other country has the Amateur population upon which it can depend for financial support? To send a delegate to an I.T.U. conference is one thing, and an expensive one at that, so that any interim regional conference appears, in the foreseeable future, to be rather difficult to achieve.

Nevertheless this Executive will do all in its power to continue the liaison with other societies, and believe that close contact by correspondence is the first step in getting organised. Apart from the problem of international frequency usage, there will be many side benefits from a closer exchange of views.


For example, how many Amateurs in this country know the licensing and regulatory provisions in other countries? So what? How will that affect me, and in any case what good will it do me? Perhaps a direct answer cannot be given right now, but it would be foolish to pretend that one cannot learn a new wrinkle from someone else, and when it comes to operating privileges, take a look at what JA Amateurs have to work with.

In any event, this Executive will be pursuing the suggestion of the A.R.S.I. most avidly, with the hope that in the end, we, in Region III. will be better equipped to face the problems in the years ahead.

PETER D. WILLIAMS, VKJIZ, FEDERAL SECRETARY, W.I.A.

CONTENTS

Matters Mobile	3	Correspondence	13
Overlay Transistors	8	Sideband	15
The Fatal Current	9	Gateway of India Award	15
Monimatch Mark 3 and 4	11	DX	17
New Call Signs	12	Experimental F.M. Station for Victoria	17
Errata—Eye Reporter	12	Federal and Divisional Monthly News Reports	19
An Appreciation	13		
Trade Review: Great Circle Map	13		

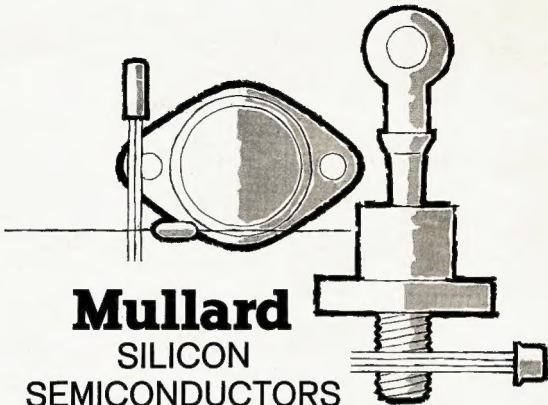

Mullard

SILICON SEMICONDUCTORS

USED THROUGHOUT THE WORLD

SILICON ZENER DIODES

230mW to 75W dissipation
4.3V to 75V nominal zener voltage

SILICON TRANSISTORS

100mW to 130W dissipation
0.45Mc/s to 350Mc/s frequency

SILICON RECTIFIER DIODES

75V to 800V maximum crest working reverse voltage
0.2A to 150A maximum mean forward current

THYRISTORS

100V to 700V maximum crest working reverse voltage
4.7A to 70A maximum mean forward current

BRIDGE-CONNECTED RECTIFIER DIODE STACKS

125V to 760V maximum DC output voltage
20A to 150A maximum mean output current

BRIDGE-CONNECTED THYRISTOR STACKS

7.5A to 117A maximum mean output current
250V to 1050V maximum DC output voltage

HIGH VOLTAGE MODULES

2kV to 18kV maximum crest working reverse voltage
0.5A to 3.75A maximum mean output current

SILICON JUNCTION DIODES

25V to 400V maximum peak inverse voltage
Up to 100Mc/s switching frequency

Mullard

MULLARD-AUSTRALIA PTY. LTD.

35-43 CLARENCE STREET, SYDNEY, N.S.W., 29 2006. 123 VICTORIA PARADE, COLLINGWOOD, N.S. VIC., 41 6644.

Associated with
MULLARD LIMITED, LONDON



M165A

MATTERS MOBILE*

A Review of Circuits and Information of Particular Interest to Mobile Operators

PAUL HARRIS, G3GFN

WHILE the contents of this series will mainly be of interest to mobile operators, such is the nature of our hobby that no one section can be completely divorced from the others. Thus it is quite probable that those who have no active interest in mobile operation may find items of circuitry and ideas worthy of inclusion in fixed station equipment.

The object is to publish circuits and technical information, together with wrinkles, dodges and hints which either improve the performance of equipment under mobile conditions, or aid operating efficiency. In addition, any matters pertinent to mobile operators' interests will also be covered. Thus the scope will be wide.

Our hobby permits almost unlimited individuality in the construction of equipment. From this it seems reasonable to suppose that there must be hundreds, possibly thousands, of useful ideas, novel circuit arrangements and unusual "bits"—bits from this and bits from that—permutations which, while of potential interest to many, have never been published. This is probably especially true of the mobile brigade where nearly every installation is tailor-made for the vehicle concerned.

The purpose of this preamble is to suggest that if you have any tested circuits which are unusual and of value to your fellow mobile operators, and you are prepared to pass on the benefit of your ideas and experience, then why not send them to your magazine for inclusion?

All that is needed is a reasonable description and, where applicable, an easily understood circuit diagram or sketch. Particularly welcome will be photographs of equipment and installations.

A HALTER MICROPHONE

The recent hiatus over the Ministry of Transport's proposed order to make it an offence to talk into a radio transmitter whilst in control of a moving vehicle, must, if we are to be honest with ourselves, at least have caused us to carefully re-appraise our operating methods.

While talking when driving can hardly be more hazardous than listening to a normal car radio, there is no doubt but that some mobile microphones do leave a lot to be desired. There can be no argument against the statement that if one hand is engaged in holding a microphone, and perhaps pressing a p.t.t. switch at the same time, then under certain conditions, one's ability to steer is affected. Anyone who has tried to negotiate a sharp turn, or a roundabout, while using such a microphone will not dispute this statement.

A microphone arrangement which goes a long way to solving this difficulty is that used in most radio taxis. In this, the microphone head is mounted either on a swinging arm or a length of swan neck tubing. Even this is not perfect for although it leaves both hands free for control of the car, the driver has to maintain his head in a fixed position, and this restricts his field of vision. It has been argued that this is less serious than having one hand engaged, but this is debatable.

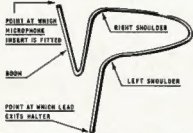


Fig. 1.—General view of the combined halter and microphone mounting boom.

Some three years ago, the writer was shown an ingenious idea by G3KLM which has all the advantages of a fixed boom microphone, but solves the problem of having to maintain one's head in a fixed position.

The device is shown in Fig. 1. From this it will be seen that it takes the form of a halter which is worn around the neck, and which incorporates a microphone mounting boom, the boom being positioned so that the microphone head is adjacent to the mouth of the wearer. No matter how much the wearer moves or turns, so the boom mounted microphone follows and maintains its proximity to the mouth.

In addition to this advantage, since the microphone lead is run through the centre of the boom, this is kept out of harm's way.

The gadget is fabricated in one piece from a length of $\frac{1}{2}$ " diameter copper tubing—obtainable from all plumbers' suppliers. The U section of the halter goes around the neck of the wearer with the straight section running down the left hand side of the chest. On the right hand side, there is another, but shorter, downward running section which bends upwards again. At the point where this commences to rise, that is at the bend, it is angled so that its top is central to the U. This will then position the microphone head—which is fitted to this rising piece—adjacent to the wearer's mouth.

Any of the usual inserts may be fitted to the boom, and the lead routed through the tubing in the manner described. Once correctly shaped to the satisfaction of the individual, the

gadget may be chromium plated, but just as good is to carefully wrap it with plastic insulation tape.

Compared to arrangements based on headphone bands, or frames of glasses, this halter leaves one virtually unencumbered. Incidentally, the writer has found that this assembly is very pleasant to use when operating a fixed station.


The only real disadvantage with this idea is that p.t.t. is not possible, but compared to its advantages, this is a small price to pay. However, it would be feasible to include a transmit-receive switch in the assembly by mounting this in a small box fitted to the end of the halter from which the lead exits.

A SIMPLE NOISE LIMITER

Apart from i.f. noise silencers, one of the most effective noise limiters is the T.N.S.—Twin Noise Squelch—circuit featured in the "CQ Mobile Handbook". Unfortunately, requiring two valves to achieve its performance, it does not enjoy the popularity which it deserves under mobile conditions where the expenditure of every extra millilamp, has to be very carefully considered.

The writer recently tested the circuit of a series limiter used in the Eico 760 Citizens Band Transceiver. Whilst the T.N.S. still has the edge, this circuit far excels any others so far tried. Of particular interest is the manner in which it handles ignition noises. They virtually disappear. Needing only one valve, one half of which is used as the detector anyway, this limiter is ideal for inclusion in mobile receivers.

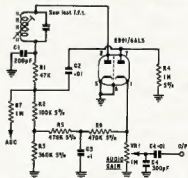The circuit is shown in Fig. 2, and as will be seen, one gets a lot for a little. The circuit not only functions as a detector and a limiter, but also provides fast attack a.g.c., itself most desirable under mobile conditions. No particular comment should be needed



ARRIVING EARLY MARCH

THE 1966 EDITION

★ A.R.R.L.—Radio Amateur's Handbook

The Standard Manual of Amateur Radio Communication

Price \$6.10 posted, or 58/6 and postage 2/6

BOOK YOUR ORDER NOW!

NOW AVAILABLE—

★ The Radio Transistor Handbook

by Stoner & Earnshaw.

Price \$6.65 posted, or 64/9 and postage 1/9

THIS UP-TO-DATE HANDBOOK COVERS A WIDE RANGE OF COMMUNICATION
FOR BOTH AMATEUR RADIO & COMMERCIAL APPLICATIONS

MCGILL'S AUTHORISED NEWSAGENCY

Established 1860


183-185 ELIZABETH STREET, MELBOURNE, C.1, VIC.

"The G.P.O. is opposite"

Phones: 60-1475-6-7



SWAN ELECTRONIC EQUIPMENT

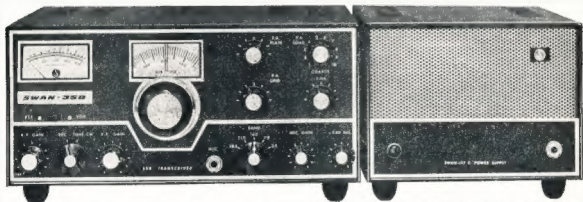

As the SWAN DISTRIBUTORS and WARRANTY STATION for AUSTRALIA, W.F.S. ELECTRONICS SUPPLIES CO. carry out all warranty claim work on SWAN equipment.

For your benefit, for our own and Swan Electronics Corporation records, and so that SWAN Service Topics and SWAN Service Bulletins can be forwarded, please advise: Name and address of owner, and model of your SWAN equipment. Upon receipt of this information you will be placed on the SWAN mailing list.

W.F.S. ELECTRONICS SUPPLIES CO.

227 VICTORIA ROAD, RYDALMERE, N.S.W.

Phones 638-1715, 638-1355

on the circuit, except to observe that close tolerance resistors must be fitted in the positions shown.

Constructionally, there are some points to watch. First, the valve-holder must be of low-loss insulation to prevent noise pulses leaking across it and so bypassing the limiter. Secondly, the valve should be fitted with a screening can, and thirdly, R1 and C4 should take the shortest possible route between the i.f. transformer and the anode of V1a.

Since the circuit is self adjusting, there is no need to incorporate a limiter on-off switch. As such switches invariably lead to leakage between input and output of a limiter, so degrading performance, if they can be omitted, then so much the better. If you should experience audio distortion to any degree with this limiter, it will be because the other fellow is riding his modulation far too hard. At 100% modulation, clipping just starts.

AERIAL MOUNTING

For those who like mobile aerial installations, neat and reasonably unobtrusive, the Ekco car radio aerial type CA225/4 will be of particular interest.

The base of this unit, which may be wing or scuttle mounted, is moulded in low-loss polystyrene, the underside of which is fitted with a stout rubber gasket, making it water-proof. The 200 ohm co-axial cable fitted to the unit when it is supplied may be easily removed, and 75/80 ohm, 50 ohm or 35 ohm cable substituted.

The special feature of this aerial is that the mounting base may be retained on the car by the use of an additional half-nut, so allowing the top section to be removed at will. For those who have "getting-in-the-garage" trouble, this is a boon. In addition, if you operate on more than one band, say 160 mx and 4 mx for example, then different aerials may be mounted on the same fitting by merely screwing them on to the protruding threaded stud. In the case of the two bands cited, on 160 mx a base loading coil would be fitted first, and the extending sections of the aerial to the top of the loading coil. When on 4 mx all that is needed is to fit the extending sections in the normal manner, and then draw them out to the optimum length.

One other advantage is that when away on holiday, or if you have to street park overnight, then the aerial can be removed easily.

WIRING HEATERS FOR 12V. AND 6V. OPERATION

Many items used for mobile are restricted in use simply because the heater circuits are wired for operation on 12v. only, and it is not always convenient, or possible, to provide this voltage in the home station.

For many years the writer has been wiring the heater circuits of his mobile equipment so that it can be operated on either 12v. or 6v. One advantage of this arrangement is that when testing newly constructed gear, this can be done by bringing into service an existing power supply in the fixed station. The mobile equipment can therefore be operated from the fixed station

should the need ever arise, and furthermore, such a facility can avoid duplication of equipment.

This facility is provided by arranging the heater wiring of the valves in a balanced series/parallel arrangement according to Fig. 3.

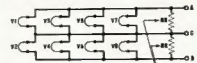


Fig. 3—Universal heater wiring allowing the optional use of 6 volt or 12 volt supply.

First, the individual heater currents are noted, and then the valves are arranged in a manner similar to that of Fig. 3 so that the total current of the valves connected between points A and C is equal to the total current of the valves connected between points C and B.

Now unless you are particularly lucky, the current in the arm AC will not equal that in the arm CB. To balance the currents, a ballast resistor will have to be fitted to the side which is short of current to make up the deficiency.

With 12 volts applied between AB, and with the currents balanced, there will be 6 volts between AC and 6 volts between CB. From this it will be seen that the ballast resistor will have to dissipate the current difference at 6 volts. From Ohm's Law, the value of the ballast resistor may be determined. The working wattage will be $W = I^2 R$, where I is the difference current. To ensure reasonably cool working, the resistor fitted should have a wattage rating of at least three times that derived from the foregoing calculation. One word of warning! Do be sure that the ballast resistor is fitted to the side of the circuit which is short of current.

In use, terminal B is connected to chassis. When operating on 12 volts, C is left open, and the supply connected to A. For operation on 6 volts, A is connected to chassis—along with B—and the supply taken to C.

If one of the valve heaters becomes open circuit, then the current of this valve will be shared by the remaining valves in its arm of the circuit. Rarely, if ever, will this cause any damage. Under such circumstances, since the equipment will not operate correctly, one is left in no doubt as to the fact that there is a fault.

When valves with a centre tap are used, such as a 12AX7 for example, one live pin is wired to A, the other to B, and the centre tap to C.

NOTABLE DOUBLES

Two valves in one envelope are always of interest to the mobileer for they save current, heat, and cost. One particularly useful little valve is the ECF82 which combines a triode and pentode in one envelope. The triode when used as an audio voltage amplifier will give a stage gain of about 60, and performs very well as either a crystal or variable frequency oscillator. As for the pentode, having a slope of 5.2 mA/v, it makes a good i.f. amplifier, or r.f. amplifier on the lower

frequencies. In transmitter service, the pentode shows high efficiency as a doubler or trebler, but in this class of operation, care must be taken to ensure that the screen grid dissipation is not exceeded.

An example of the circuitry which can be woven around this valve is shown in Fig. 4. This is a crystal oscillator and multiplier sequence for a 4 mx transmitter, and will give 1.5 mA. of drive through a 22K ohm resistor in the grid of a 5763 p.a. running 9 watts input. Thus two valves, an ECF82 and a 5763, will make up into a very compact, low power, 4 mx transmitter.

The American number for the ECF82 is 6U8. It has been noted that a 6U8A has recently been introduced, and from information available, this appears to be an improved version of the 6U8.

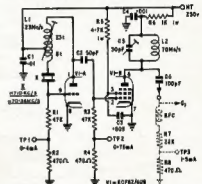


Fig. 4—Single valve 70 Mc. driver. L1, 31 turns 28 s.w.g. enamel, close wound on 1/4 in. former with iron slug. Tap at eight turns. L2, seven turns 18 s.w.g. air wound 1/4 in. inside diameter. Turns spaced 1/8 in. apart. TPI, T2 and T3 indicate currents to be expected between test points and earth. Components shown dotted are self circuit of following stage.

THIEF-PROOFING EQUIPMENT

As some of us know to our cost, merely locking a car is not sufficient to deter a determined thief.

Since having been through the bitter experience of having equipment stolen, the writer has incorporated the following arrangement in his car. While it does not stop a potential thief getting at the equipment, nor from taking it out, once it is moved, even fractionally, from its correct position, the car horn sounds, and nothing can stop it. The resulting din is more than enough to deter a thief who, above all, does not want attention drawn to himself.

The circuit arrangement is shown in Fig. 5. Its operation relies on the fact that the equipment is securely mounted, and that the back of the equipment presses on a microswitch firmly fitted either directly to the bodywork of the

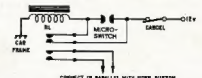


Fig. 5—Burglar alarm circuit. The "cancel" switch is normally ON. To stop the alarm, this switch is opened.

JOYSTICK

VARIABLE FREQUENCY ANTENNA 1.5-30 Mc.

The world's most versatile and compact h.f. band antenna for transmission and reception. More than 4,000 stations throughout the world are equipped with the Joystick and associated A.T.U. Testimonials pour in, takes a kilowatt and favours the DX. Overall length 7 feet 6 inches.

ORDER NOW!

Joystick Antenna, standard make (aluminium elements)	£17/7/0
Joystick Antenna, de luxe make (all copper elements)	£19/9/0
Joymatch A.T.U. Type 2 for receive only on b.c. bands	£5/15/0
Joymatch A.T.U. Type 3 for receive and transmit (low power and mobile)	£3/15/0
Joymatch A.T.U. Type 5 for transmit only (rated 150 watts)	£2/10/0
Mobile Mounting Kit (converts existing Joystick for mobile mounting)	£3/13/0
RF40 Field Strength Meter (magnetic base, 1-250 Mc. coverage)	£6/19/6

Send for descriptive literature and testimonials, including the outstanding performance of the Joystick used by ZL4GA who W.A.C. in one day and QSO'd G6WV and VETBII on 3.5 Mc. WJOE says the Joystick equals half-wave dipoles and similar conventional antennae on 160, 80 and 40 and has proven superior to them in the 15 and 30 metre bands.

PENNANT IMPORTS (ELECTRONICS) CO.

P.O. BOX 26, BEECROFT, N.S.W.

CHOOSE THE BEST—IT COSTS NO MORE



G. T. LEMPHREY & CO. LIMITED. Head Office: 27-41 Bourdon Street, Alexandria, N.S.W.
and at Melbourne • Brisbane • Adelaide • Perth

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)
Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)
Telegrams: "Metals," Adel.

LOW DRIFT CRYSTALS

FOR

AMATEUR BANDS

ACCURACY 0.01% OF
STATED FREQUENCY

3.5 and 7 Mc.

Unmounted, £2/10/0

Mounted, £3/0/0

12.5 and 14 Mc.

Fundamental Crystals,

"Low Drift"

Mounted only, £5.

THESE PRICES DO NOT
INCLUDE SALES TAX

Snot Frequency Crystals
Prices on Application.

Regrinds £1/10/0

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY, E.7,
VICTORIA

THE NEW "A.R."

LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages
with more writing space.

Price 7/6 each
including Postage

Obtainable from your Divisional
Secretary, or W.I.A., P.O. Box 36,
East Melbourne, C.3, Victoria.

car, or to an arm anchored to the bodywork. If the equipment is moved, then the microswitch operates and sets off the alarm. At this stage it should perhaps be mentioned that the microswitch is of the "press-to-open" variety.

The operation is not quite as simple as has been described for the circuit as is so arranged that even if the equipment is restored to its correct position, the horn does not cease to operate. It just goes on and on and on and on . . . This interlock is quite vital. For ease of circuit tracing, the primary wiring has been illustrated in heavy lines, while the interlock is shown in lighter lines.

The heart of the arrangement is the double pole relay fitted with contacts which close when the relay is energized. The primary circuit starts from the negative terminal of the battery and runs through the alarm-cancelling switch, and then through the microswitch to the relay energising coil to the frame of the car. As it stands at the moment, and with the equipment in position, the microswitch is pressed and in the off position. If the equipment is withdrawn, the pressure on the microswitch is released, the circuit completed, and the relay closes. One set of contacts on the relay wired in parallel with the horn button completes the horn circuit. At this stage, if the equipment is returned to its correct position, or the leads to the microswitch cut, then the horn would cease. To avoid this, an interlock is provided. This is achieved by arranging the second pair of contacts on the relay to be in parallel with the microswitch; thus once the relay is closed by the action of the microswitch, one set of the relay contacts maintain it locked "on".

To stop the alarm you either have to know where the cancelling switch is located, or dive under the bonnet to disconnect the battery—and no thief will hang around that long.

The value of this alarm switch depends on how the cancelling switch is concealed. Disguising is often better than hiding, and in the writer's car it is in full view of anyone who enters.

SHOESTRING MODULATION

The writer is always intrigued by descriptions of modulators which, for d.c. inputs of 15 watts or less, employ push-pull modulating valves. On Top Band, or for any transmitter with a d.c. input of less than 15 watts, there is no need to go to such lengths to modulate the carrier in a satisfactory manner.

Taking Top Band as a practical example, a single 6BW6 will, if allowed to do so, run an input in excess of the legal limit. The interesting thing about the 6BW6 valve is that its impedance as a p.a. for 10 watts input (40 mA. at 250 volts) is near to its optimum load impedance as a single ended output stage for the same value of h.t. supply. The figures are: p.a. impedance, 6.2K ohms; optimum load impedance, 5.5K ohms at Va and Vs of 250 volts. Since the 6BW6 as an audio output valve will deliver 5.5 watts, this is quite enough power to fully modulate a p.a. input of 10 watts. Indeed, under speech waveform conditions, and a reasonably accurate match, the audio output is likely to be quite a bit higher.

Using these facts, gleaned from the valve manufacturers' data, considerable simplification becomes possible. The principal advantage is derived from the fact that the modulation transformer needs only have a 1:1 ratio, and where this ratio is required, with the arrangement to be shown, a full blown modulation transformer is quite unnecessary.



Fig. 6—Method of using centre-tapped audio output transformer as a modulation transformer.

The circuit is shown in Fig. 6. In this a standard centre tapped audio output transformer is used in such a manner that, as far as the p.a. is concerned, it "looks" like a modulation transformer. The transformer has to fulfil two requirements: the impedance on either side of the centre tap should be equal to, or near to, the desired impedance—in this case between 5.5K ohms and 6.5K ohms; each half of the winding must be able to carry the current expected to flow through it. Many such transformers are freely available, and moreover, at a cost far below that of a "normal" modulation transformer.

If the equipment in which this idea is incorporated is a transceiver, then the modulating valve can be arranged to do double duty and serve as the output stage of the receiver. Under these conditions the speech coil winding on the transformer can be coupled to a loudspeaker in the normal manner. Naturally, arrangements have to be made to mute the loudspeaker during transmission, and in addition, the transmitter switching should be arranged so that the cathode of the p.a. is disconnected to avoid the p.a. valve acting as a diode connected to the far end of the output transformer while receiving.

While the 6BW6 has been specifically cited, this method is not restricted to this valve alone, neither is it essential that the p.a. and modulating valves are of the same type. Many combinations are possible as a study of valve data will show.

This system has been used by the writer in various low power transmitters and transmitter/receivers. There have never been any reports of under-modulation or poor quality. Quite aside from its advantages circuitwise, it materially assists in getting the proverbial gallon into the pint pot.

FIELD STRENGTH INDICATOR

One problem faced by all mobile operators, irrespective of the band on which they operate, is to monitor the level of r.f. radiated by the transmitting aerial. It is neither practical, nor accurate, to use a field strength meter inside the car to determine what is going on outside.

One way round this is to use an external aerial coupled to a F/S meter inside the car, but unless one is prepared to have aerials sprouting out all over the place, hardly ideal.

A neat way of overcoming the need to fit a special aerial is to use a wing mirror as the pick-up for the internal F/S meter. All that is needed is to insulate the wing mirror from the bodywork of the car, and then run a lead from the fixing nut into the car.

On the l.f. bands this can be a plain lead, but on 4 m.x. co-axial cable should be employed. If both l.f. and v.h.f. operation are undertaken, a co-axial lead should be fitted, but without earthing the outer braiding at either the mirror or the salon ends. When used on the l.f. bands, the F/S meter should be arranged so that the inner and outer of the co-axial cable are connected together, thus turning it into a plain lead. On v.h.f., the F/S meter should be arranged to treat the lead as normal co-axial cable.

A method of bushing a wing mirror for this purpose is shown in Fig. 7.

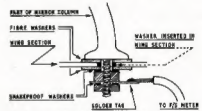


Fig. 7—Insulating a wing mirror to allow it to be used as the aerial for a field strength meter.

MICROPHONE HEAD AMPLIFIER

Most of the diminutive inserts of Japanese origin—such as would be suitable for the halter-boom for example—have impedances ranging from 25 ohms to 250 ohms, and so require the use of a matching transformer. By the use of a single transistor in a suitable pre-amplifier, such a transformer may be dispensed with, and in mobile working this has certain advantages.

The pre-amplifier shown in Fig. 8 was designed specifically for microphones with this range of impedances, but of greater interest, employs a couple of "ideas" so that, although it is positioned at the microphone head, only a single screened lead is needed to (a) bring the output from the pre-amplifier to the main amplifier, and (b) take the supply up to the pre-amplifier.

The first circuit oddity to note is that the forward bias is taken from the collector. This forward bias is thoroughly decoupled by R3 and C2 so that

(Continued on Page 8)

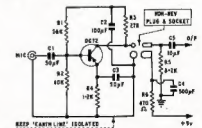


Fig. 8—Microphone pre-amplifier for inserts with an impedance of between 25 ohms and 250 ohms. This unit may be constructed in a small metal clip-on case and used as a co-axial in-line amplifier.

MATTERS MOBILE

(Continued from Page 7)

none of the output at the collector is fed back into the base of the transistor. By using this arrangement, one lead is dispensed with, namely that usually needed to take the supply to the forward bias circuit.

The second oddity relates to the input circuit on the main equipment. Either a co-axial socket can be used, in which case it must be fully insulated from the chassis, or a two-pin non-reversible socket with matching plug as shown on the diagram. The inner lead of the screened cable goes to the main amplifier via the capacitor C5. The resistor R5 is the load for the transistor collector circuit, which, it should be noted, runs from the live tag on the socket to chassis negative (earth). The screen of the cable is not earthed in the usual manner, but only earthed for signal currents by C4. The screened outer of the cable is continued, via the resistor R6 to a source of 9 volts positive. In point of fact, any voltage between 6 volts and 9 volts can be used, and this circuit has been arranged so that the source of this voltage is the cathode of one of the valves in the main equipment across whose cathode bias resistor this voltage exists. From this it will be appreciated that there is no need to arrange a separate supply for this pre-amplifier.

One point which will be apparent is that the screening of the linking cable is positive with respect to the chassis and other metalwork of the equipment

by the supply voltage to the pre-amplifier. Thus the linking cable must be provided with a sheath over its braiding. If this braiding does become shorted to chassis or the metalwork, then it will short-circuit the supply to the transistor. Since the source voltage for the transistor comes from the cathode of a valve, under these conditions the valve would be running without bias. To protect against such an eventuality, R6 is included in series with the supply source so effectively preventing damage to the valve concerned.

☆

OVERLAY TRANSISTORS

A new emitter electrode structure called the "Overlay" was first used commercially in the power transistor 2N3375. This transistor, introduced in 1964, has 156 emitters tied together in parallel by diffused and metallised regions. This approach provides a considerable increase in the emitter edge-to-area ratio and a proportionate reduction of the input time constant. This has permitted a practical transistor with a 3 watt output at 400 Mc. or 7.5 watts at 100 Mc. for 1 watt drive.

The production of this type of transistor is exacting and very tricky, which accounts for its present high cost. In lots of 1,000, the price is around \$14.

Another type, the 2N3866, used for u.h.f. driver applications, has 16 emitters each 0.15 mils. wide by 2 mils.

long. Due to a reduction in input capacitance, the frequency response has been improved and the unit has a minimum gain of 10 db. at 400 Mc. for 1 watt of output power. It sells in lots of 1,000 for about \$3.

There are a number of the well known companies now producing these devices, and types range from 50 watts at 50 Mc. at 28 volts, through 10 watts at 400 Mc. at 28 volts, to 1 watt at 800 Mc. at 28 volts. A number of the types operate on voltages around 12 to 14 volts and prices are in the vicinity of \$28.

Although the overlay transistor appears to be the answer to v.h.f. and u.h.f. semiconductor devices for some time to come it may still be out of the price range for the average Amateur unless quantity requirements and production techniques improve to make them cheaper.

☆

ARMY AMATEURS

A recent issue of "Army" the Army newspaper, carried an article on official Army Amateur Stations, i.e. those authorised by the Army using Army equipment operating in various parts of Australia and in overseas theatres. A list of these were nominally being VKA 3UW, 3UF, 3AHF, 3AAS, 3AIF, 3ZVC, 4CS, 2FV, 1RM and 8QJ. In addition to these ten official stations, there are, of course, many Army operators using their own equipment scattered throughout the Commonwealth.

It is always pleasing to note when a Government Service uses it to promote the art and make available equipment for the pursuance of a hobby which knows no bounds.

American "Dage" Standard V.H.F. CO-AX CONNECTORS

(As used widely in "QST" and "CQ" circuits and on disposable equipment)

- PL259 Co-ax Plugs (PTFE) ... 9/9
- SO239 Co-ax Sockets (PTFE) ... 9/9
- UG-175-U Adaptors, adapts PL259 Plugs to range of Co-ax Cable diameters ... 3/3
- C30-14 Co-ax Couplings, couple two PL259 Plugs (PTFE) ... 17/6
- C30-17 " " Co-ax Joiner (PTFE) ... 25/6
- (Useful for sampling r.f. in transmission line for c.r.o. measurement.)
- C30-16 Right Angle Co-ax Connector (PTFE), male to female ... 18/9
- (Prices include Sales Tax)

"JABEL" TR-14 REAMERS

Ideal for clean finish on small panel holes and cleaning out for neat fit.

Price: 10/6 each.

F455-FA-21 FILTERS

COLLINS Type F455A Mechanical Filters, 455 Kc. Wiring instructions with each unit.

Price (inc. S.T.): £17/10/0

AIWA M-18 CRYSTAL MIKES

For use into ½ meg. load or higher, ideal speech range 500 c/s. to 7 kc., output -32 db.

Price: 79/6

TRANSMISSION LINE EQUIPMENT

Formula III Low-Loss 300 ohm open wire Transmission Line. 100 ft. lengths, coiled and boxed. Price £1/1/9 (inc. S.T.)
14 gauge hard-drawn Copper Wire for Amateur Antenna Systems. Any length cut. Price 7d. per yard (inc. S.T.)
Porcelain Egg-type Insulators. Price: 18/- doz. (inc. S.T.)

PENETROX "A"

Famous American aluminium and copper corrosion inhibitor. Avoids bad electrical connections and corroded joints on beam antennae, t.v. antennae, etc. Use—

PENETROX "A"

Price: 10/- per tube
(Post Paid)

QUALITY SCREW DRIVER SET

ORIENT No. 3350 Screw Driver Set with wall-holding rack. Set includes one each 3, 4, 5, 6, 8 in. plus 4 in. Phillips head.

Price: 18/- set

HAVING T.V.I. TROUBLE?

A "CAUTION" Low Pass Filter will fix it! Cut-off frequency, 30 Mc.; attenuation at 60 Mc., better than 30 db.; insertion loss, negligible; impedance, 50-75 ohms.

Price: £5/15/0 (inc. S.T.)

KIKUSUI MODEL 539 3" C.R.O.

240 a.c. operation. Printed Circuit Board wiring, 5 c.p.a. to 1 Mc. time base oscillator sweep 10 c.p.a. to 100K c.p.a. in steps with continuous in-between variation. Ideal s.b. measurement with coupled r.f. sampling signal. Weight, 11 lbs.

Price: £55 plus 12½% S.T.
(Full instruction book supplied)

GELOSO KIT FOR D.S.B. TRANSMITTER

The following components comprise the GELOSO Kit for construction of D.S.B. Transmitter. For circuit details refer Nov. '65 issue of "Electronics Australia".

- 4/105 Crystal controlled Beat Frequency Oscillator ... £12/10/0
- N.1697 Calibrated Dial, Pointer and Escutcheon ... £2/16/0
- N.4/113 Pi-Coupler ... £2/3/0
- N.771 Condenser ... £1/19/6
- N.774 Condenser ... £1/19/6
- N.17634 All Wave R.F. Choke ... 8/6
- All plus 12½% Sales Tax.
- Valves not supplied with VFO.
- Valves for VFO: 6U8, 6AH6, 6CL6.

WILLIAM WILLIS & CO. PTY. LTD.

428 ELIZABETH STREET. MELBOURNE, C.I

Phone 34-6539

The Fatal Current

C. O. BRAINARD, WA0JBU

STRANGE as it may seem, most fatal electric shocks happen to people who should know better. Here are some electro-medical facts that should make you think twice before taking the last chance.

IT'S THE CURRENT THAT KILLS

Offhand, it would seem that a shock of 10,000 volts would be more deadly than 100 volts. But this is not so. Individuals have been electrocuted by appliances using ordinary house currents of 110 volts and by electrical apparatus in industry using as little as 42 volts direct current. The real measure of a shock's intensity lies in the amount of current forced through the body, and not the voltage. Any electrical device used on house wiring can, under certain conditions, transmit a fatal current.

While any amount of current over 10 Ma. is capable of producing painful to severe shock, currents between 100 and 200 Ma. are absolutely lethal. There is no known medical procedure that will revive the victim.

Currents above 200 Ma., while producing severe burns and unconsciousness, do not usually cause death if the victim is given immediate attention. Resuscitation, consisting of artificial respiration, will usually revive the victim.

From a practical viewpoint, after a person is knocked out by an electric shock, it is impossible to tell how much current has passed through the vital organs of his body. Artificial respiration must be applied immediately if breathing has stopped.

THE PHYSIOLOGICAL EFFECTS OF ELECTRIC SHOCK

Voltage is not a consideration in the physiological effects of various current densities. Although it takes a voltage to make the current flow, the amount of shock-current will vary, depending on the body resistance between the points of contact.

Shock is relatively more severe as the current rises. At values as low as 30 Ma., breathing becomes laboured, finally ceasing completely even at values below 75 Ma.

As the current approaches 100 Ma., ventricular fibrillation of the heart occurs (an unco-ordinated twitching of the walls of the heart's ventricles). There's no worldly help for the victim.

Above 200 Ma., muscular contractions are so severe that the heart is forcibly clamped during the shock. This clamping protects the heart from going into ventricular fibrillation, and the victim's chances for survival are good.

DANGER—LOW VOLTAGE

It is common knowledge that the victims of high-voltage shock usually respond to artificial respiration more readily than the victims of low-voltage shock. The reason may be the merciful clamping of the heart, due to the high current densities associated with high voltages. However, lest these details be misinterpreted, the only reasonable conclusion that can be drawn is that 75 volts are just as lethal as 750 volts.

The actual resistance of the body varies, depending upon the points of contact and the skin condition (moist or dry). Between the ears, for example, the internal resistance (less than skin resistance) is only 100 ohms, while from hand to foot it is closer to 500 ohms. The skin resistance may vary from 1000 ohms for wet skin to more than 500,000 ohms for dry skin.

GENERAL SAFETY PRECAUTIONS FOR YOU

When working around electrical equipment, move slowly. Make sure your feet are firmly placed for good balance. Don't lunge after falling tools. Kill all power and ground all high voltage points before touching wiring. Make sure that power cannot be ac-

identally restored. Do not work on ungrounded equipment.

Don't examine live equipment when physically or mentally fatigued. Keep one hand in your pocket while investigating live electrical equipment. Above all, do not touch electrical equipment while standing on metal floors, damp concrete, or other well-grounded surfaces. Do not handle electrical equipment while wearing damp clothing (particularly wet shoes) or while skin surfaces are damp.

Remember, the more you know about electrical equipment, the more headless you're apt to become. Don't take unnecessary risk.

WHAT TO DO FOR VICTIMS

Cut voltage and/or remove victim from contact as quickly as possible, but without endangering your own safety. Use a length of dry wood, rope, blanket, etc., to pry or pull the victim loose. Don't waste valuable time looking for the power switch. The resistance of the victim's contact decreases with time. The fatal 100 to 200 Ma. level may be reached if action is delayed.

If the victim is unconscious and has stopped breathing, start artificial respiration at once. Do not stop resuscitation until medical authority pronounces the victim beyond help. It may take as long as eight hours to revive the patient. There may be no pulse, and a condition similar to rigor mortis may be present; however, these are manifestations of shock and are not an indication that the victim has died.



9th Brunswick Scout Troop, Donald Street, Brunswick (Vic.) during the Jamboree-on-the-Air on 16th and 17th October. Left to right: Alan Westwood, Jan Sardi, Jeffrey Patterson, Brian Patterson, Michael McDonald, David Fellow. Front: Dawn Westwood (L.C.M.) and George Robertson (VK3WJ).



WARBURTON FRANKI

● POLYPACS

Bags of Assorted Components.

\$1 each (10/-) S.T. inc.

- No. 1—30 Resistors, $\frac{1}{2}$ and 1 watt—also Presets.
 No. 2—20 Capacitors—Paper, Mica, Plastic, Ceramic.
 No. 3—20 Silver Mica Capacitors.
 No. 4—20 Styrofoam Plastic Capacitors.
 No. 5—50 Assorted Grommets (2 for \$1).

Postage—1 pac 4c (5d.); 3 pacs post free.

● PROTECT YOUR PREMISES WITH THE SCOTT ELECTRONIC EYE

- A.C. Mains Operated.
 - Kit consists of Light Source and Eye Unit.
 - Complete with power supply, amplifier, buzzer, hardware and connecting wires.
- Use across doorways or other openings up to 25 ft. wide.

\$33.33 (£16/13/4)

Plus S.T. 12½, plus postage for weight of 4 lb.

● SILICON DIODES

18 amps. at 50 p.i.v. Available **75c (7/6)**
 with either K or A to case plus S.T. 12½

1 amp. at 1,000 p.i.v. **\$1.35 (13/6)** plus S.T. 12½
 Pack and Post 5c (6d.).

● RESISTOR SUBSTITUTION BOXES

Twenty-four values from 15 ohms to 10 megohms. Selected by two rotary switches. Complete with leads and clips.

\$3.65 (36/6) plus 12½ S.T.

● CAPACITOR SUBSTITUTION BOXES

Nine values from 100 pF. to 0.22 uF. Selected by rotary switch. Complete with leads and clips.

\$2.47 (24/8) plus 12½ S.T.

● TRANSISTOR AMPLIFIER — SINCLAIR X-20 PULSE-WIDTH MODULAT. AMPLIFIER & PRE-AMP. OPEN MATRIX BOARD CONSTRUCTION

12 Transistors, size $8\frac{1}{2} \times 3\frac{1}{2} \times 1$ in. Weight 4 oz.

Input sensitivity—1 mV. into 5,000 ohms.
 Total harmonic distortion—Less than 0.1% at 10W
 Frequency response at all power levels—20 c/s. to 20 Kc plus 1 db.
 Damping Factor—greater than 100.
 Quiescent consumption—Approx. 150 mA.
 Supply Voltage—30 to 37 volts (7.5 ohm speaker).
 20 to 45 volts (15 ohm speaker).
 Output Power—7.5 ohm Speaker, 20 watts r.m.s. music power
 15 ohm Speaker, 15 watts r.m.s. music power
 Supplied with comprehensive descriptive booklet showing circuit and recommended circuitry for volume and tone controls.

\$26.50 (£13/5/0)

Plus S.T. 25%. Pack and Post 10c (1/-).

A.C. POWER SUPPLY TO SUIT—

(Will supply two Amplifiers for **\$12.60 (£6/6/0)**

Stereo use.) Plus S.T. 12½.

Pack and Post 25c (2/8).

● MULTIMETERS—200H

Fan-shaped meter movement

Ranges: DCV—3, 25, 50, 250, 2,500 at 25K o.p.v.
 ACV—10, 50, 100, 500, 1,000 at 10K o.p.v.
 DC mA—50 uA, 2.5 mA, 250 mA.
 OHMS—600, 600K.
 CAP.—10 pF. to 0.1 uF.
 DB—Minus 90 to plus 22.
 Supplied with leads and instruction leaflet.

\$9.50 (95/-)

Plus S.T. 12½ Pack and Post 15c (1/6).

● MULTIMETERS—SANWA 370X

Ranges: DCV—3, 6, 12, 150, 300, 1,500, 3,000 at 4K o.p.v.
 ACV—4, 12, 120, 300, 1,500, 3,000 at 4K o.p.v.
 DC mA—0.3, 3, 30, 300.
 DC Amps—3, 12.
 AC Amps—3, 12.
 OHMS—10K, 100K, 1 meg., 10 meg.
 DB—Minus 90 to plus 33.
 Minus 0 to plus 33.
 Supplied with two pairs of test leads and comprehensive instruction booklet.

\$26 (£13)

Plus S.T. 12½. Pack and Post 25c (2/8).

Wooden Carrying Case to suit. Well made with safety lock and removable lid.

\$7.90 (£3/19/0)

Plus S.T. 12½. Pack and Post 20c (2/-).

● MICROPHONE MIXERS

Mixes the outputs of up to 4 high impedance microphones. Separate volume controls for each mike. Attractive metal cabinet, 6 in. x 2½ in. x 2½ in.

\$7.20 (72/-) Plus S.T. 12½.



WARBURTON FRANKI

22 PARK ST. SOUTH MELB., VIC.

PHONE 30 lines **69-0151**



● **TRADE ALSO SUPPLIED**

● Please include postage and freight with all orders

MONIMATCH MARK 3 AND 4*

Much Improved Version of
a Popular Loading Indicator

DENNIS HAMPTON, ZLSJ

THOSE who are fortunate in having a subscription to "QST" will realize that I have based this article on a recent one of theirs. However, having recently constructed both models for use at work, with excellent results, I have jotted down my findings and construction details for readers.

It is most desirable that the final amplifier of every transmitter should be terminated in a purely resistive load. If any appreciable reactance is present in this load, transmitter efficiency will suffer. A direct indication of the load's reactance and resistance content is given by the standing wave ratio on the line feeding the load, i.e. the co-ax, ribbon or open wire line immediately following the transmitter.

As the majority of Amateur transmitters in current use have co-axial output, the Monimatch reflectometer has come into wide use as a matching indicator. Nearly all Monimatches, commercial and home-made, built to date, are of Mark II. variety and have two inherent disadvantages. Firstly, the meter used needs to have high sensitivity in the order of 100 microamps, to be of any practical use, and, secondly, the pick-up unit or reflectometer itself is difficult to construct and fiddly to adjust.

Both the Mark III. and Mark IV. use a 1 mA. meter, and their pick-up units can be assembled in a few minutes, with no adjustment necessary if reasonable care has been taken.


In addition, the sensitivity of both units is better than older models—the simpler but less sensitive Mark III. required at 40 Mc. an output power of 0.3 watts to obtain full scale meter deflection on the forward power reading. If a 100 micro-amp. meter had been used, 3 mW. would have sufficed to obtain a maximum reading. The Mark IV. required only 4 watts output at 3.5 Mc., whereas at 14 Mc. it would handle 80 watts—a larger pot would enable greater power to be handled. Thus the Mark IV. has several times the sensitivity of the older Mark II. r.f. power meters (calibrated dummy loads were used here for the above tests.)

It is essential that the diodes be matched and are available in matched pairs. Alternatively, a suitable pair could be had by placing several diodes of the same type, one by one, in a simple r.f. absorption circuit. Two diodes, giving the same meter reading at several scale points, would be matched. Both circuits and their operation are identical to the Mark II.

CONSTRUCTION


Apart from the cabinet (approx. 5" x 3" x 3", 16 gauge aluminium—depends on component sizes), the whole job can be completed in under two hours.

* Reprinted from "Break In," Sept. 1968.

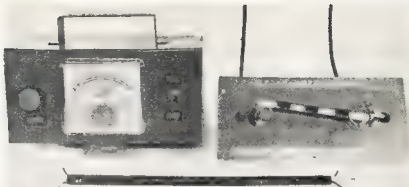

The pick-up units are made by stripping the sheath and braid from RGS/U co-ax and binding, with p.v.c. tape, the pick-up wires on either side of the bared co-ax. It is important that these wires are snug against the side of the co-ax. The Mark IV. unit is taped for its whole length, whereas the Mark III. is taped at each end and in the middle.

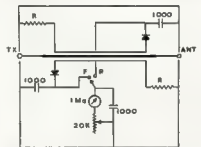The co-ax unit is then connected between the input and output sockets or three lug terminal strips. Keep the terminating resistor and diode leads as short as possible and endeavour to keep the completed unit symmetrical—attention to this and the snug pick-up wires will ensure a balance of voltages of the forward and reflected power readings.



The Mark IV. pick-up unit can be bent into an "S" for mounting in its box with little effect on performance.

Mark III.:-

Co-ax 4 1/2", 14 gauge wire 3 1/2".

Terminating resistors:

For 50 ohm line, 470 ohms.

For 75 ohm line, 430 ohms.

Mark IV.:-

Co-ax 1 1/4", 14 gauge wire 10 1/2".

Terminating resistors:

For 50 ohm line, 270 ohms.

For 75 ohm line, 220 ohms.

If desired, the meter, pot and switch can be built into a separate box and coupled to the reflectometer box by a plug, lead and socket. This could be desirable if there were several tx/ant. set-ups in the station. Another variation would be the use of the reflectometer box with pot and switch only, used with an external multimeter—what could be cheaper?

CALIBRATION AND TESTING

The meter is calibrated by the following formula:

$$SWR = \frac{F + R}{F - R}$$

where F is the scale reading of forward power.

R the reflected power.

Example: If the forward reading is 1 mA. and the reflected 0.5 mA., $SWR = (10 + 5) \div (10 - 5)$ or 3:1. If reflected power is 0, SWR is 1:1, if it is 1 mA. (i.e., same as forward) SWR is infinity to 1. The meter can be re-calibrated by carefully scraping off the old markings with a sharp knife, and marking appropriate SWR points in Indian ink.

To check that the device is balanced, connect it into the transmitter line, switch to forward, and adjust the reading for a point near full deflection. Note this reading. Reverse the input and output connections, switch to reflected, and note the reading. If both readings are the same, or close (say ± 0.2 mA.), the reflectometer is balanced. If not, one of the pick-up wires will have to be moved away a little from the side of the co-ax, till balance is achieved.

Both units built here required no adjustment. To identify the switch positions, terminate the line in a dummy load—the reflected power will always be lower than the forward power.

When using the indicator resonate the transmitter final, and adjust the forward power reading for full scale deflection. Switch to reflected and read off the SWR . In use, the aerial or tuning unit should be adjusted for maximum forward and minimum reflected power—generally these will tend to coincide. If the transmitter power is adequate, it is advisable to leave full loading till antenna adjustments are completed. Put out just enough power to operate the SWR indicator.

PARTS REQUIRED

- 1 matched pair of OA81, IN34 or similar diodes.
- 1 20K \pm w. pot.
- 1 1,000 pF. disc ceramic capacitors.
- 2 terminating resistors—should be high stability, non-inductive and at least 5% tolerance.
- 1 S.p.d.t. switch.
- 1 0-1 mA. meter.
- 2 Co-axial sockets or 3-lug tagstrips.

NEW CALL SIGNS

OCTOBER, 1966

VKQRM—R. Stacey, 4 Hanover Avenue, Epping.
VKPZP—W. R. Treloar, 23/5 Pullerton Street, Woolahara.
VKJRS—D. S. Jeanes, "Villa Maria," Ayr.
VKZDX—R. R. Coutts, Hastings Road, Castle Hill.
VKZTO—R. O'Connell, 2 Bridge Street, Eastliff.
VKZOB—K. E. Overly, Station Hotel, West Coast, Postal: 388 Illawarra Road, Murrumbidgee.
VKZET—T. Mitchell, 81 Roslyn Street, Burwood.
VKZNV—S. B. Backhouse, 35 Moore Street, South Caulfield.
VKZVA—P. Winters, 28 Robyn Drive, Nunawading.
VKZAA—N. W. Deague, 26 Somers Avenue, Malvern.
VKZAB—J. A. Moran, R.R.I.S. No. 1, Aircraft Depot, R.A.A.F. Laverton.
VKZAC—St. Anne's Science Club, St. Anne's Church, of England Girls' Grammar School, 8 Raymond Street, Sale.
VKZAC—Scotch College Radio Club, Scotch College, Glenferrie Road, Hawthorn.
VKZAL—A. W. Holt, 38 Longana Ave., Glenferrie.
VKZAM—G. Harrison, Chapman, The Vicarage, Flinders, Victoria.
VKZAN—A. Howie, Salisbury Ave., Werburton.
VKZAO—A. D. Swinton, 780 Waverley Road, Glen Waverley.
VKZAP—P. T. C. Morrison, C/o Forests Commission, Mt. Taylor.
VKZAQ—F. Williams, 30 Powlett Street, East Melbourne.
VKZAS—M. L. W. Park, 14 Rosemont Avenue, Burwood.
VKZAS—D. H. Murray, 9 Myrton Street, Burwood.
VKZAW—Warrambol Technical College Radio Club, Grattan Road, Warrambol.
VKZBX—J. L. Lakey, 113 Panton Street, Golden Square, Bendigo.
VKZBR—A. C. Ryan, 4 Adamson Street, Braybrook.
VKZBS—F. D. Dixon, 8 Empire Street, East Preston.
VKZBG—L. A. Goding, 15 Yarrabee Court, Mt. Waverley.
VKZBL—A. M. MacLean, 157 Charman Road, Mentone.
VKZBN—R. L. Waite, 48 Seymour Road, Elsternwick.
VKZBV—N. Huld, 73 Bayswater Road, Croydon.
VKZVL—Gertrude Williams, 30 Powlett Street, East Melbourne.
VKZYN—J. H. Young, 100 Glenholm Street, Mitchelton.
VKZDY—W. Dalgleish, 25 Crawford Street, Redcliffe.
VKZFP—F. W. Chapman, 17 Shaftesbury Street, Exbury.
VKZHH—E. Hall, 16 Kailworth Street, Sherwood.
VKZQT—Teachers' College Radio Club, Victoria Park Road, Kelso Grove.
VKZFD—A. M. Dunn, 308 Woodford Road, Elizabeth North.
VKZKO—J. B. Lewis, Caroline Road, Square Mile.
VKZIM—S. J. Mahony, 19 Kentish Road, Elizabeth Downs.
VKZJK—B. F. Brockhouse, 158 First Avenue, Royston Park.
VKZMR—M. W. Reiger, 26 Cromer Parade, Mullewa.
VKZRD—R. Gordon, 24 Seventh Avenue, Cheltenham.
VKZRE—G. A. Johns, 25 Wallace Street, Balaklava.
VKZYM—W. J. Mordue, 8 Shearer Street, Myra.
VKZNN—D. Ross, 46 Norma Road, Alfred Cove.
VKZOM—D. A. Hancock, Flat 7, 198 Labouchere Road, South Perth.
VKZAK—W. P. Kent, 16 Rowley Street, Brighton.
VKZAN—E. G. Smith, School Quarters, Walkaway.
VKZDC—P. J. Beecher, 81 Egan Street, Kalgoolie.
VKZFO—J. Q. Sullivan, 4 Anthony Street, Palmyra.
VKZFR—L. Jones, R.A.A.F. Base, Pearce.
VKZMB—A. C. McBurnie, 29 Benjafield Terrace, Mount Stuart.
VKZMD—D. R. Marsland, 16 Nimbin Street, Montague.
VKZNF—R. J. Wirth, Station: 4 Eleventh St., Lee, Postal: C/o Box 251, P.O., Lee.

VKZRA—R. H. Ashley, Christmas Island, Indian Ocean.
VKZAV—J. B. Masters, 44 Eden Street, Stuart Park, Darwin.
VKZMR—M. D'A. Richardson, 18 Mary Street, Stuart Park, Darwin.

NOVEMBER, 1966

VKIYG—G. Yanow, 23 Carrington Street, Deakin.
VKIAP—A. E. Peppercorn, 43 Higginsbotham Street, Turin.
VKIZG—C. J. Cashion, 63 Jamesbotham Street, Watson.
VKZNB—W. J. Guthrie, Lot 1, Dalton Road, St. Ives.
VKZUK—E. Klein, Postal: P.O. Box 158, Liverpool: Station: 14 Yaranabool Street, Mt. Prichard.
VKZAJ—W. J. Lark, 9 Cosimo Street, Old Toongabbie.
VKZAY—C. S. Smith, 46 Wyuna Road, Fyrmby.
VKZAP—Merrylands Amateur Radio Club, 81 Hanbury Street, Merrylands West.
VKZBC—Camp Technology Amateur Radio Club, Station: Mt. Victoria: Postal: 18 St. Aidan's Avenue, Dundas.
VKZBP—J. Fernu, 11 Milton Avenue, Mosman.
VKZBQ—J. E. Clark, 30 Dazling Street, Chiswick.
VKZBR—G. Gibbons, 135 (Lot 4) Bull Road, Wentworthville.
VKZBK—W. P. F. H. Schroeder, Marshall Street, Dora Creek.
VKZBK—K. J. Callaghan, Flat 3, 28 Coolah Street, Griffith.
VKZBR—K. R. Brackenbury, 18 Perkins Street, West Ryde.
VKZBV—R. B. Broad, 3/7 Bogota Road, Crenshaw.
VKZBD—J. Bedford, O.T.C. Wireless Station, Fivisville, via Ballan, Victoria.
VKZBQ—D. I. Sulett, 8 Lurbar Street, Noble Park.
VKZBF—F. J. Miller, 43 Gordon Street, Stones Corner.
VKZBM—M. P. Moody, 77 Bayview Terrace, Clayfield.
VKZBK—R. Kilworth, 1 Johnston Street, Carleton Place.
VKZBF—M. J. Fisher, 23 Searle Road, Appleton.
VKZBT—F. Talbot, C/o Tracking Station, Carmarvon.
VKZBF—W. Talbot, C/o Tracking Station, Carmarvon.
VKZBR—L. Gunther, 76 View Street, Sandy Bay.
VKZAF—A. E. Humphreys, Wilkes.
VKZBK—K. C. Martin, Mawson.
VKZRM—C. R. Lebbon, Mascarete Island.

ERRATA—PYE REPORTER

Errors in Circuit Diagram, "A.R." Nov., '65, page 4 and sheet distributed by Victorian Division.

John Haseldine, VK5JC

1. Cathode bypass (25 μ F. 25v. electrolytic) of V8 (6AV6) omitted.
2. 0.1 μ F. and 47 ohm (in parallel) below and between V8 and mic. transformer: as drawn, this shorts out the negative supply by earthing same. The capacitor value should be 0.01 μ F. The negative line from the power supply should connect to the junction of the 47k, 47 ohm and 0.01 μ F. The 47 ohm and 0.01 μ F. return to earth. Note. The negative supply is the voltage drop across this 47 ohm and the 39 ohm in the power supply—said resistors being in parallel.
3. The suppressor grid of V9 (audio output and modulator) is internally connected to the cathode. It is shown wrongly as an external connection.
4. A wire wound resistor (1.5k Ω .) has been omitted between the "break" contact of the "B" changeover group (Rel. 1) and the 47k anode load of V8.
5. P.A. anode metering. A 2 μ F. capacitor is incorrectly shown across the 10 ohm resistor which is in series with a 3k resistor. Starting at the "B" contacts on the relay, the order that the components should be shown on the circuit are as follows: the 10 ohm resistor in series with the 3k resistor to the winding on T7, the 2 μ F. capacitor is in parallel with the 3k. The meter leads are: H.T. to pin 7 on SK1 and the junction of the 10 ohm and 3k resistors to pin 5 on SK1.

CRYSTAL DIVISION

Manufacturers of Quartz Crystals for Frequency Control and Crystal Filters for Highly Selective Circuits announce:—

NEW! LOWER PRICES FOR CLOSE TOLERANCE GOLD PLATED CRYSTALS FOR AMATEUR APPLICATIONS

- | | Amateur Net (each incl. Tax) |
|---|------------------------------|
| • 1.2 Mc. to 14.999 Mc. $\pm 0.005\%$ in Style "D" holders, $\frac{1}{2}$ " pin spacing | £2 8 6 |
| • 15 Mc. to 47.999 Mc. $\pm 0.005\%$ in Style "D" holders, $\frac{1}{2}$ " pin spacing | £2 10 6 |
| • 48.0 Mc. to 61.0 Mc. $\pm 0.005\%$ in Style "D" holders, $\frac{1}{2}$ " pin spacing | £2 16 3 |
| • 100 Kc. $\pm 0.005\%$ in HC13/U holders, $\frac{1}{2}$ " pin spacing* | £4 10 0 |
| • 1 Mc. $\pm 0.005\%$ in Style "D" holders, $\frac{1}{2}$ " pin spacing* | £4 10 0 |
| *Specialty designed for Crystal Calibrator purposes. | |
| • 455 Kc. nominal Crystals for Filter applications in Style "D" or "E" (B7G) holders | £4 10 0 |

Many other types and tolerances are available from our standard production. Please consult us on your Crystal requirements.

PYE PTY. LTD. CRYSTAL DIVISION

1A KILPA ROAD, MOORABBIN, VIC. Phones 95-2011, 95-6741
STATE OFFICES IN ADELAIDE, BRIERBANK, HOBART, PERTH AND SYDNEY

AN APPRECIATION

AUSTRALIAN BOY SCOUTS ASSOCIATION

2nd December, 1965.

Australian President of the Wireless
Institute of Australia,
Mr. G. M. Hull,
22 Dryden Street,
Canterbury, E.7.

Dear Mr. Hull,

I am writing on behalf of the Australian Boy Scouts Association to convey our thanks to the Wireless Institute of Australia for the splendid help and co-operation which its members gave to the Boy Scouts Association in all parts of Australia during the function known as the 8th Jamboree-on-the-Air.

We have received reports from all parts of Australia which indicated the great success of the function and the enthusiasm that it was received by the many Scouts and Girl Guides who took part.

At the present time we are not in a position to report exactly how many took part in the Jamboree-on-the-Air but we do know that it was a record and that even greater enthusiasm than that shown previously attended this year's function.

The Jamboree is only made possible because of the great interest and assistance of your members and we would be pleased if by some means you could convey to them this expression of our thanks on behalf of the whole association.

We look forward to continued co-operation in the years that are to come and would like you to know that in the Scout Movement there is a growing enthusiasm for this event.

With best wishes to your Institute and the good work that it is doing.

Yours sincerely,

E. M. Derrick, National Secretary.


Trade Review

GREAT CIRCLE MAP

We are pleased to have had the opportunity of examining a great circle map published by our friends, Mullard-Australia Pty. Ltd.

The map, based on Sydney is 22 in. in diameter, printed on heavy paper 26 in. x 36 in.

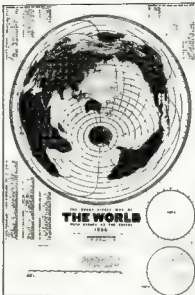The countries are marked with their prefixes, and major cities are pinpointed.



There is a cut-out scale, in English miles, which, by locating at a marked pivot point, can be used to measure mileage to any part of the world.

Over 300 countries are listed, with prefixes, on three corners of the chart. The fourth corner is used for a world time calculator, using a cut-out disc.

By spending very little time mounting this map on hardboard you will have a most attractive and useful adjunct to the shack.

It is a must for the DX man, who will easily adapt it to his beam direction indicator.

At 10/- (\$1) plus 2/- (20c) for packing and postage, nobody should be without it.

Orders, enclosing remittance, should be addressed to Mullard-Australia Pty. Ltd., 35-43 Clarence Street, Sydney, N.S.W.



Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the publishers.

DUTY ON AMATEUR EQUIPMENT

Editor "A.R.," Dear Sir,

I agree resoundingly with Mr. Bliss in his conclusions reached in this column (January issue), but would point out that I am well and truly familiar with preferential Commonwealth import duty rates, and so is the Customs Office in Hobart, from whom I obtained the information published here. I merely did the various calculations including the prescribed rate of sales tax as applicable. It is a silly point, and far more important is the problem of the crushing customs duties which are imposed on Amateur equipment brought to Australia. The issue is certainly not solely that of protecting Australian industry; perhaps it is simply a matter of a lucrative and reliable source of income for the government. In that event, we should not hold our breaths until reasonable duties are imposed on non-competitive equipment.

—R. L. Gunther.

F.V. CLUB

9 Rothwell Tce., North Glenelg,
South Australia.

Editor "A.R.," Dear Sir,

At the time of writing this letter there are 48 members of the British Amateur Television Club in Australia and New Zealand, six in S.A., eight in VK1, five in VK2, four in VK3, two in VK7, and one at present in VK5 though several applications for membership in S.A. will be forthcoming in the near future.

As the editor of "Amateur Radio" is a complementary member, I thought of approaching him to find out if there was sufficient interest among our far-flung T.V. fans in Australasia to form a sub-group affiliated with the club so as to facilitate interchange of technical ideas and also to buy major components from the parent organisation.

For those who may be interested in joining the club, although British by name, is international with about one-third of its nearly 1000 members living outside the United Kingdom in a large number of countries including America. It publishes a quarterly magazine, "CO-TV," which is free to members. Direct membership costs £125 or 11/8 Australian (16/- sterling). Though subscriptions through a locally organised branch would be probably slightly more in order to defray the postage costs involved.

This suggestion is partly my own idea, and partly that of an officer of the club, and it would be in our interest if we felt such a scheme likely to succeed that it be forwarded to London as soon as possible for approval by the committee.

I have sent a copy of this letter to the Club Secretary.

For anyone interested in joining, I hold some membership application forms.

—C. R. W. (Dick) Ashton.

★

CONTEST CALENDAR

12th/13th February. — John Moyle Memorial National Field Day Contest (Rules Dec. "A.R.").

19th/20th February. — R.S.G.B. 1.8 Mcs. Contest.

19th/20th March. — B.E.R.U., 1966 (Rules "R.S.G.B. Bulletin," Sept., 1965).

Phone 34-6539, write or call

WILLIS & Co Pty Ltd.

423 Elizabeth St., Melbourne

for **GELOSO**
Equipment and Components

JOHN MOYLE MEMORIAL NATIONAL FIELD DAY CONTEST, 1966

12th February to 13th February

A. R. R. L.

Associate Memberships (and renewals) are available by forwarding £2/14/- (plus 6d. interstate cheques) to:

Business Manager, W.I.A.,
49 Cookson Street,
Camberwell, E.8,
Victoria.

This includes the regular arrival of

"QST"

GALAXY or SWAN, what set to buy if you want to go all-band s.s.b. with commercial equipment?

The answer is not difficult. If you only plan to contact your friends on your own frequency and little else, let the more attractive appearance of the SWAN's decide. But if you want more versatility work dx on your own frequency or follow a drifting station with an external v.f.o., check sideband suppression for your friends or the other sideband of an s.s.b. station, the GALAXY offers more at a saving. Including sideband selection as standard equipment, adding an externally plugged-in crystal calibrator and VOX unit, and an external v.f.o. will cost \$160.00, less with a Galaxy V than in the case of a Swan 350 Mark III. What is more you should be able to construct a satisfactory single-range external v.f.o. yourself, a near impossibility with a Swan 350 as it must perk on 8 12 16 and 22 Mhz. Also, you do not need a v.f.o. adaptor for a Galaxy and sideband selectors and calibrators are not kits of components to be wired in.

Anyway, both makes are excellent transceivers, the cheapest all-band s.s.b. sets on the market and they still cost \$600, including a heavy-duty 240 v a.c. supply/speaker combination in matching cabinet. The a.c. supplies use a separate transformer for the 200 v supply where loads vary up to 200 watts on peaks. The only way to maintain maximum regulation for proper linear operation of the antenna including bumper or body mounting assembly is \$48. Just one mobile antenna tuneable to any frequency between 3.5 and 30 Mhz. To work dx you need a little more than a G5RV as antenna and HY-GAIN offers many possibilities. 10/15/20/40 meters vertical 14AVQ, \$44. 10/15/20/40/80 meters vertical 18AVQ \$78 (must be guyed—32 ft tall). Yagi beams, 10 to 20 meters junior TH3JR, \$85 10 to 20 meters TH3Mx2 "Thunderbird" \$140. Other models on special order. Two 14AVQ verticals make an excellent 4-band dipole as a basis for a super Yagi beam.

ROTATORS for Yagi beams. For junior models the ALLIANCE U-88 is adequate, \$35, for average size beams use a CD TR 44 \$100. The C-D HAM-M will carry maximum loads, costing \$170.

For the man who wants to or needs to roll his own, there are still plug-in crystal filters, vernier dials and vernier assemblies, 50 mmid s.f.c. condensers, gangable with extension shafts, co-ax connectors and switches. 7000-7180, 8000-8100 and 8895-9000 Kcs., FT 243 crystals, \$1.50.

AUTOMATIC transistorised automatic keyers, with built-in monitor and power supply, no relays, \$70.

USE COLLINS KWM-2, in excellent condition, with Collins PM 2 110/220 v a.c. supply-speaker unit and stable home-made external v.f.o., \$1000.

5-band Transceiver with 240 v a.c. supply/speaker
USB-LSB Sideband Selection
Crystal Calibrator
Full-range external v.f.o.
v.f.o. adaptor
VOX

SWAN
SW 350 M-III
25 kit
25 kit
160 model 420
40 model 22
45
\$895

GALAXY
model V
included
10
90
not needed
35
\$785


SIDE-BAND ELECTRONICS ENGINEERING

P.O. BOX 23, SPRINGWOOD, N.S.W.


Telephone: Springwood 51-1394

Importer of GALAXY, DRAKE, AZTEC, GONSET, HY-GAIN, SWAN Distributor

TRIMAX for a complete transformer range!

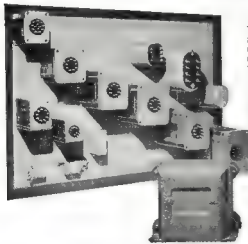

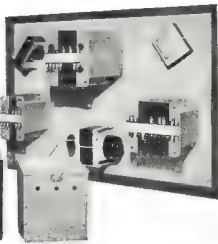Trimax have available most types of transformers, ranging in weight from a fraction of an ounce to half a ton. You bring us the problem—we will supply the transformer.



L M ERICSSON PTY. LTD.

"TRIMAX" DIVISION

FACTORY, Cnr. WILLIAMS RD. & CHARLES ST., NORTH COBURG, VICTORIA. PHONE: 35-1293. TELEGRAPHIC ADDRESS: "TRIMAX" MELB.



L M 51

SLIDEBAN

Sub-Editor PHIL WILLIAMS, VK3NN

S.B. TRANSCEIVERS (Continued)

Apart from American transceivers the most notable is the British KW-3000 which has features to satisfy the British user. It has 50w. p.e.p. rating with a single 8445 output stage, being sufficient to drive a linear amplifier to the full 850w. peak input permitted by English regulations. Most U.S. transceivers head at least twice this drive larger linear amplifiers to their U.S. legal limit, which accounts for the higher general input level of 200w. or more for most of the previously mentioned units.

Inclusion of the 160 mc band was essential for British operating conditions, with a 40w. peak input power restriction for s.b. transmitters. While on the subject of the 160 mc band, I must ask why more VK slideband operators do not use this band. I have heard of only two others, VK3AVA and VK3BEM besides myself who have used the band with our full 150 watts. Anybody with the usual 9 Mc. slideband generator and 5.0 to 5.5 Mc. v.f.o. can get on 160 mc merely by doubling the v.f.o. to 10.8 Mc. and subtracting 8 Mc.—the mixer will do all the doubling you need, without your help and the only thing left for the operator is to put the class A and A1 band linearly tuned circuits on 1.8 Mc. An 85 mhz. GERNY adapter will do the job beautifully against ground (use the back yard water pipes) and you are there. Contacts with U.S.A. may be somewhat more difficult now than when WAGNER was active, but ZLA are quite easy to contact.

But to get back to the KW-3000 series made by Rokeby Sherris, G8KX. Those who have known me for some time will know that I am a sucker for a little high when purchased in Australia, but if you can get one brought back by a friend or relative—complete with v.f.o. power pack, even the "girt" duty does not make the cost unreasonable. This KW-3000, with its limiter, is recently being advertised as the "G-line". Its slideband is obtained from a mechanical filter and it has all of the modern features such as a.i.e.

The Australian production of an s.b. transceiver in N.S.W. has not materialised, as far as I am aware, and I say this because I do not know. I have heard several reports of one on the air, but it would seem that small scale local production could match the U.S. high volume production. The publicity I have seen and the signals heard from this Wagner unit seemed to indicate that the unit was first class and the two v.f.o.s. included a standard was an excellent idea for the Australian Amateur. The s.b. transceiver under construction at VK3NN will include this idea for which I thank Messrs. WAGNER.

Hallcrafters have recently brought another tri-band transceiver, the 8R-500, on to the market. It will take a peak input power of 500 watts with 15 db. a.i.e., making this the highest-powered self contained unit available.

Units most commonly available to the Australian Amateur for purchase in this country are those made by Collins, Hallcrafters, Swan and Galaxy Heathkit and Elecraft and are available with quite a saving in monetary outlay.

It is unfortunate that the Heathkit, Slideband Engineers and Transcom units will not tune the Australian frequency assignments in the 30, 40 and 20 mc bands. So some re-wiring, splitting and dia. re-calibration will be necessary before use in this country.

There is no doubt that the transceiver is becoming the most popular piece of equipment for operating mobile when on long journeys or even just travelling to work, and also for those who like to operate in the bush and warmth from the living room instead of a cold and noisy shack.

The transceiver units mostly finish up with three or four valves in the v.f. output section, one ast. mixer, class A stage, and output class A1 stage. Those who have operated are excellent performers in the receiving mode, with negligible battery drain.

Before leaving the commercial scene, I must mention one more manufacturer of "separators" which may be made to transceive, viz. Divco. This is a new firm which advertises its DR-30 fully transistorised receiver and companion DT-20 transmitter which is yet to be seen and

is still coming. The interesting thing about these units is their weight and size, the receiver weighing 9 lbs. and is 7 x 6 x 8 inches, and the transmitter 7 x 9 x 11 inches.

The home construction of s.b. transceivers is not an impossible task and the writer has a transistorised version with a 9 Mc. crystal filter under construction. The availability of cheap n.p.n. silicon transistors with adequate high frequency characteristics makes this a completely practical proposition. Transistorised v.f.o.s. even in valve type equipment has enabled single mixing to the final frequency from say 5 or 9 Mc. a.s.b. generators. The temperature drift problem with valves is not present to the same extent.

The manufacture of good six-crystal h.f. filters complete with carrier crystals will assist the home constructor, as this is one of the most difficult items to be "found". I am producing an Australian crystal manufacturer to get his prototype filter fixed up ready for production. The six-crystal job is better for reception than the four-crystal filters which are commonly used for transmission. The side-job "pop-ups" can be troublesome for receiving. I'm sure we all wish this filter manufacturer the best of Amateur luck with this project.

More detailed data may be obtained from equipment reviews in "QST", "CQ", "73", and S.G.B. magazines. Perhaps some of these and the advertisements will help with the selection of your gear.

Because of the small quantities of imported gear sold in Australia, no importer is going to grow fat on the profits made from amateur s.b. sales. The field is competitive and everybody sees the overseas prices in the magazines.

For those whose age or health preclude them from construction of complicated gear, the purchase of an s.b. transceiver will prove a bit of "ease-of-life" and ensure enjoyment of contacts which are just so easy using s.b.

In future issues it is hoped to be able to discuss the companion linear amplifiers which are available, as well as s.b. transceivers and transmitters for the v.h.f. bands.

73 for now, Phil VK3NN.



GATEWAY OF INDIA AWARD

The Gateway of India Award is sponsored by the Amateur Radio Society of India, Western Zone, in memory of the late Rev. R. Conna, S.J. (VY3SK), the founder and first secretary of the Western Zone. This attractive certificate is available to all licensed Amateurs of the world and may be claimed by working the following:

(a) Applicants in Asia to work ten Amateurs in the Western Zone.

(b) Applicants in the rest of the world to work five Amateurs in the Western Zone. All contacts must have been made on or after November 9, 1957, the day on which the Western Zone was founded. There are no band or mode restrictions and there are no endorsements.

The Western Zone comprises the States of Madras, Mysore, Patiala and Kerala, and the Laccadive Islands. Contacts with Amateurs who have moved out of, or were temporarily in, the Western Zone are also valid for this award, provided their QTHs are clearly indicated on the QSL cards.

QSLs are NOT required. Send certified list signed by another Amateur or by a club official, together with six I.R.C.s (for DX Amateurs) to the Awards Manager, Dady R. Rajagopal, 281 The White Mansion, 55 Sleater Rd., Bombay 7, India.

AMATEUR FREQUENCIES:

USE THEM OR LOSE THEM!

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY AND OUTPUT

Our Crystals cover all types and frequencies in common use and include overtones, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U:

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:—

6280, 4095, 4535, 2760, 2524 Kc.

5.500 Kc. T.V. Sweep Generator Crystals, 23/12/6
100 Kc. and 1000 Kc. Frequency Standard,
28/10/6 plus 12½ Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, £6/10/0 each plus 12½ Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 AND 7 Mc. BAND.

Commercial—0.02% 23/12/6, 0.01% 23/15/6, plus 12½ Sales Tax.

Amateur—from £3 each, plus 12½ Sales Tax.

Regrids—Amateur £1/10/0, Commercial £1/17/6.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrel, Box 2102, Auckland.

Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

46 Eastgate Street, Oakleigh, S.E.12, Vic.

Phone: 57-6387

With the co-operation of our overseas associates our crystal manufacturing methods are the latest



SWAN NEWS!

SWAN SW350 Mk. 1, Mk. 2, ??????

As the SWAN DISTRIBUTOR for Australia we are finding this crop of Mk's quite confusing, especially as the latest Mk. III as listed by a retailer is quite unknown even to the Swan Electronics Corporation themselves.

To clarify this matter the history of development is as follows:—

The original SW350 encountered slight drift troubles in SOME UNITS only, also some click trouble was evident on c.w. No dial set trimmer was fitted and only partial coverage of the 10 metre band was available.

The SWAN Corp. in their continued programme of improvement have fitted ceramic formers and improved temperature control in the v.f.o., this modification overcame the drift. They then fitted a new dial and added full coverage on 10 metres, they also fitted a dial set trimmer on the front panel as standard and anti-click circuitry.

To differentiate between this model and the earlier model this company added the Mk. II to the model number.

Since these changes a different crystal filter of module form has been fitted. As no difference in operation is evidenced no further Mk. number has been used for this model which is still known in Australia as the SW350 Mk. II.

As can be seen from the above the SWAN Corporation are continually developing their equipment to give the Amateur the finest equipment available regardless of cost.

You just can't go wrong with the SWAN SW350 or SW400 Transceivers and accessories

W.F.S. ELECTRONICS SUPPLIES CO.

227 Victoria Rd., Rydalmere, N.S.W. 638-1715

ATLANTIC RADIO

36 Oxford St., Woollahra, N.S.W. 31-7811

FOSTER DYNAMIC MICROPHONES FOR HAND-DESK USE

SPECIFICATIONS:

Output Impedance	...	50 ohms or 50K ohms
Effective output level	—55 db. [0 db. — (one) 1V. Microbar]	
Frequency response	...	200 to 10,000 c.p.s.

OMNI-DIRECTIONAL DYNAMIC:

SIZE: 3" x 2-1/8" x 1".
Cable: 12 ft. of P.V.C.
Switch: on-off.
Desk Stand. Clip folds for hand use
Colour: WHITE.
Plastic Diaphragm.

Retail Price

50K ohms

£2/14/0

+ Sales Tax 4/9

A QUALITY PRODUCT OF EXCELLENT DESIGN

DF-2

Marketed by ZEPHYR PRODUCTS PTY. LTD.

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556

Manufacturers of Radio and Electrical Equipment and Components

Agents: D. K. Northover & Co.; Neil Muller Ltd.; Homecrafts (Tas.) P/L; Jacoby, Mitchell & Co. P/L; T. H. Martin P/L.





Sub Editor: ALAN SHAWSMITH, VK469
35 Wynnot St., West End, Brisbane, Qld.

Firstly, a word or two on that perennial question: "The state of the bands?"

21 and 28 Mc. After showing signs of promise, have like the gentler sex, turned coquette and withdrawn their attentions. The bands are at present down on last month's form.

20 mx is now far and away the "top of the five." Good DX and opening during the night hours. South Africa and Europe after 1900s.

For 7 Mc. the ionosphere is not being very indulgent. The S.R. to Europe from 1800s is a chancy business indeed. QRM from Asian commercial on this dog-watch is colossal. A check on the first 30 Kcs. of 40 mx at 1900s on 8/13/58 showed very approx. 18 stations other than Amateur. This makes the band at this time of early morning almost useless for DX.

NOTES AND NEWS

Eastern Island: C2CAC appears around 0900s on odd days.

Islands: Gen. 5X3PB worked 14,000 Kcs. 2000s. Says QSL direct to P.O. Box 436, Honolulu.

Manitoba: Roul VK1AI on regularly and easy to QSO. Try 14 c.w. after 1300s.

Tough: 2ZBSE said to be working 30 c.w. Try around 1700s.

Nauru: Lloyd WK6G using the prefix K6G8Z or VK9 should be very active from here by the time this reaches you. QSL VSAAC Foundation.

Lacedaive: J1 VU9NR and VU9AK are making plans to activate this rare spot. More information if the project comes to realization.

Laurel: LA6FG is said to be on 16,400 Kcs. at 1600s.

Malaysia Rep.: 5REAM on 14,000 at 1830s-14,000 or 14,100 active.

Philippines: 8F3USA on quite often around 14,000 after 1300. QSL W7WTD.

Kuwait: 8E3AN, 14,000 at 1830s.

North Borneo: W6ML a regular on 14 Mc. after 1000s. Says QSL via bureau.

Elites: J1: VR1S active from Fianafuti 0730s, 14,000 and 14,100.

Syria: VK1AA reported QRV 1300s. 14,000.

S.A.E. and IGC: Call Book QTH.

British Republic: Jack, TY1ABT is said to be active on 14,400 s.a.b. at 1300s.

Spanish Morocco: EABAZ seems to be authentic. Try 21,200 daily at 1630s.

Tahiti: J1: F0BET will be QRT sometime late March or early April. But will work all bands actively till then. Mode A1 and QSL to 21M.

Feet Tights: C2SAP and C2RAE both QRV almost nightly. 14,800 Kcs. at 1300s or later.

QSL to D.M. Port Timor: 14,000.

Honduras: VR4CR is said to be still active. A.m./c.w. mostly 14 Mcs. QSL to Weather Office.

Cayman: Ian 48T1W and Denver 48TDA are both very active. The former 14,200 s.a.b. at 1300s and the latter on 7 and 14 Mcs. c.w.

Switzerland: ZDER, 14,118 at 1300s. QSL VEOAK. Also reported here in VK on 21 Mc.

Yugoslavia: PLACIC on QSL to 8R5KC. Spontaneously. Both A1 mode around 14,970 after 1300s.

Central Is.: Lou, W5EYB will be on again from this spot off the Mexican coast probably February. Call will be XE3. Freq. 21.410 and higher. Good for WPX only.

Kerguelen: New QTH.

Names: Eric and Peter, s.a.b. men but use c.w. also. Acredy they have been heard on several frequencies on QSL to 8R5KC.

Sedan: ZT888 on 14,200, 14,600. QSL to J. Collins, USAID, American Embassy, Khartoum.

Mail Reg:

Czelet: Alois has a new op., Jean Pierre, 1832s at 14,150. Call is FB5WU.

Falklands: W5R2Z, 14,220 at 0500s.

8 Islands: LU1ZC, 14,200 and 14,600 at 2000s. QSL to RCA.

Don: Miller, W5WNV, plans expeditions to the virtually unknown but well salt yet! spots in Oceania as well as FWA Wallis and Manahiki. He is now fast out from ZK3 but will have departed to fields anew by the time this reaches you. Keep listening on 7, 14 or 21 for the pile-up. His signals are usually strong and there never was a better operator.

ACTIVITIES

Rae VK5TL, who quietly picks up the choice ones each month, worked the following on 20 mx: A Quad 80 ft. high is going to put out a "Big Sig." for Ken on the base. He worked on 20 mx C2RKG, C2RAE, C2KAAU, F1AA, F1AMC, H2R3G, K2TMO, H2CE, ITIRAL, K2GIC, K2RMC, H2R4N, M1A, M2MOP, V2PUP, V2PJK, V2P2D (SL K2H), V2P5R (Grand Turk), V2P7K, V2Q8PA (Agale), V2S0C, X2WGA (Aeromob), V2V7A, V2V8A, Z2CAM, Z2RYV, Z2T2G, Z2T3A, V2Z3CM (40 m.), 5813R, 5247D, 4115R, 5N1M, 9G1FR QSL's received were Z2P7C, X2WGA, 4115R, 5813R, 5247D, Z2B1A, H2MCO, P2P5A, Z2P5S, O2D3G, V2P7Y, V2V7A, X2K3H and more.

Bud VK1MY, who runs 150 w. into a G.F., picked up some nice ones this month on c.w. viz. P2Y2BIR 090, VQ3AI 1455, K2R3C 700, U2QH0 030, CX1RY 110, 0M2ZY 180, V2S0C 1322, K2C5E 070, F1AMC 1820, K2R3AN 1333, H2W14 140, SX2U 140, SF2U4 15002, Y2UTAN 2145, V2V8A 0550, C2RAE 1400, Y2C3B 0700.

Chas. VK4UC, before leaving for a Gold Coast vacation logged the following: U2R4D 1200, H2B4AD 1230, ITA1Q 1330, F2P5BQ 1440, X2W5BD 1450, 40 m. 1830, K2R3C 1830, 40 m. 1730, K2W4H, K2C5E 070, 0M2ZY 0710, M2P4B7K 1300, L2IK6G 1300, U2R1B 030, H2AL 0620 QSL to Box 343, Harland, OZK. 1300, U2C3KA 1300, 40 m. 1830, K2R3AN 1333, H2W14 140, SX2U 140, SF2U4 15002, Y2UTAN 2145, V2V8A 0550, C2RAE 1400, Y2C3B 0700.

All the above times are G.M.T.

Graham, VK4AG, reports now 315 confirmed which is really a stout effort for a comparative newcomer to the game.

Trev. VK2NS, reports having chalked up 150 plus 40 m. Another 80 m. effort considering the layers of QRM on this band. More activities reports please.

QSL MANAGERS

VYR40-Q2R0 M1QJ-ON4QJ
VYR4X-VK1AEY SU1GM-Q3BYM
VYJ1A-W1RGT SV1AB-W4HUE
VYK1A-K2R3C 700, U2QH0 030, CX1RY 110, 0M2ZY 180, V2S0C 1322, K2C5E 070, F1AMC 1820, K2R3AN 1333, H2W14 140, SX2U 140, SF2U4 15002, Y2UTAN 2145, V2V8A 0550, C2RAE 1400, Y2C3B 0700.

SUMMARY

In past years commencing February at this QTH, the LP on 20 mx to Europe which takes in South America and North Africa on the way, usually improves considerably and remains so until late May. Those who find it convenient to operate from 0400 to 0900s should pick up some good ones.

Have you ever paused to consider the size and impact of Amateur Radio in the world today? The Big Fraternity, which was a few short years ago but an infant in swaddling clothes, is now somewhere near the "strong palms" stage with half a million or so of us. Within this huge framework there exists countless clubs and societies or groups in which DX activity plays a big part. Surely, with the right motives this incessant exchange of contact and ideas must lead to something more than inconsequential in the promotion of good will and understanding. We have the potential for this thing there on the desk in front of us, but sadly we do so little about it.

My thanks again to all those who regularly provide reference information. Also DX Editors LIDRA, Fin DX'er and now with Jim, GSJGT whose bulletin "Airwaves" is now received on an exchange basis. 73. A1 VK4E5S.

VKS CALLS - 1960

(Information supplied by VKEL of A.N.A.R.K.)

Macquarie Island: VK0MI, Collin Leblond (c.w. s.a.b.).

Marion: Base: VK0KM, Keith Martin (s.a.b.).

Wilkes: Base: VK0AH, Alan Humphries (s.a.b.).

In all three cases QSL via VK3 Bureau-Eric Trebilcock (13992).

John Moyle Memorial

NATIONAL FIELD DAY

CONTEST, 1966

12th and 13th February.

Experimental F.M. Station for Victoria

The Postmaster-General's Department has granted a licence to conduct test transmissions in the u.h.f. band using frequency modulation. Technical details are as follows:

Call letters: VZCY
Frequency: 554 Mc. plus or minus 0.0025%.
Bandwidth: 200 Kc.
W.R.P.: 500 watts
Deviation: Plus or minus 75 Kc. (proposed).
Pre-emphasis: 50 micro-seconds.
Polarisation: Horizontal, cross polarisation envisaged.
Modulation: F.m. monaural and f.m. stereo-
phonic.
Stereo system: F.C.C. (America) pilot tone system.
Transmitter location: The Olinda area of the Dandenong Ranges.

The purpose of the experiment is to investigate the following:—

- What are the problems associated with the use of the u.h.f. band for f.m. stereo broadcasting services?
- Is the use of elliptical polarisation to all dead spots in coverage necessary? Will it make reception practical in portable and mobile receivers?
- What are the problems associated with stereo sound S.L.A. systems when used with u.h.f. transmissions?
- What receiver design would be most suitable for u.h.f. stereo transmissions?
- To what extent is the public interested in f.m. radio services?

The experiments will not include the transmission of advertising material, or simulate commercial broadcasting in any form.

It is anticipated that pre-recorded music and speech will form part of the test conditions. It is hoped to commence transmissions shortly.

For people living in the Sydney area, we would advise that a similar experimental station is being set up in Sydney. For further information contact the Postmaster-General, P.O. Box 3968, G.P.O. Sydney, N.S.W.

As the allocated frequency is in the u.h.f. band, it should be noted that standard E.M. waves at 100 Mc. will not be suitable for reception. A newsletter is available to those who are interested. Information or comments regarding the station would be welcomed for possible inclusion in newsletter. Requests should be addressed to F.M., P.O. Box 90, Toorak, Vic.

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. New members and those whose totals have been amended will also be shown.

PHONE

Call	Car. No.	C't-ries	Call	Car. No.	C't-ries
VK5MS	34	230	VK2JZ	91	246
VK3AH	51	314	VK2ADE	65	231
VK2AB	46	312	VK4HR	12	223
VK6RU	2	310	VK2AAK	58	214
VK6MK	43	307	VK5KW	4	211
VK4FJ	31	283	VK5WL	14	211

New Members:

VK3RV	55	101
VK3TG	46	143

C.W.

Call	Car.	Cnt.	Call	Car.	Cnt.
No.	No.	ries	No.	No.	ries
VK2KD	10	320	VK4BH	71	283
VK3QL	5	308	VK4JZ	52	283
VK3XC	28	308	VK4JZ	79	285
VK4FJ	29	300	VK4AK	58	259
VK4DE	11	286	VK4EL	14	311
VK3NC	19	288	VK4XB	75	247

Amendment:

VK3RJ	45	236
-------	----	-----

OPEN

Call	Car	C't	Call	Car	C't
No.	No.	ries	No.	No.	ries
VK4ADE	28	322	VK2ACX	8	329
VK4R1	8	316	VK3NC	17	287
VK4JZ	76	315	VZ74	43	271
VK4JZ	63	315	VK4H	7	284
VK4MK	74	309	VK4RV	18	284
VK4JF	32	308	VK2APK	52	243


New Members

New Members

VK3LZ	97	115	VK4R1	88	113
-------	----	-----	-------	----	-----

F-SERIES S.S.B. EQUIPMENT by Yaesu Musen

PROFESSIONAL QUALITY AT AMATEUR PRICES

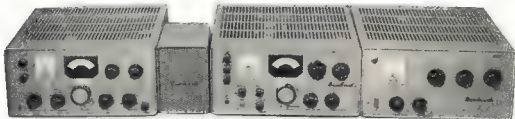

COMPACT TABLE-TOP STATION—MECHANICAL FILTER SYSTEM FIVE BANDS—80-10 METRES TRANSCIVE OR NORMAL OPERATION

FR-100B: S.s.b.-a.m.-c.w. dual conversion receiver with two mechanical filters for best reception of s.s.b. and a.m. Xtal filter for c.w.; a.n.l., a.g.c., S meter, s.s.b. clarifier, monitor, etc.

FL-200B: S.s.b.-a.m.-c.w. transmitter, 240w. p.e.p. input, with two 6JS6 tubes in p.a. running within ratings for longer life! Solidly constructed and neatly wired, with high quality components, ceramic bandswitch, Kokusai M.F., Solid State Power Supply, etc.

New, fully descriptive illustrated brochure from the Australian Agents:—

BAIL ELECTRONIC SERVICES

60 SHANNON STREET, BOX HILL NORTH, VIC.

Phone 89-2213

FOSTER DYNAMIC MICROPHONES

SPECIFICATIONS:

Output Impedance 50 ohms or 50K ohms
Effective output level -55 db. [0 db. — (one) 1V. Microbar]
Frequency response 50 to 15,000 c.p.s.

OMNI-DIRECTIONAL DYNAMIC:

Plastic Diaphragm. Swivel fits 5/8" 26 t.p.i. Stands.
Size: 4½" long, 1½" diameter. Colour: TWO-TONE GREY.
Cable: 12 ft. of P.V.C.

Retail Price 50K ohms: £4/16/0 + Sales Tax 10/0

Retail Price 50 ohms: £4/14/0 + Sales Tax 9/10

A QUALITY PRODUCT FOR TAPE RECORDERS & P.A. USERS



DF-3



Marketed by **ZEPHYR PRODUCTS PTY. LTD.**

58 HIGH STREET, GLEN IRIS, S.E.6, VICTORIA

Phones: 25-1300, 25-4556

Manufacturers of Radio and Electrical Equipment and Components

Agents: D. K. Northover & Co.; Nell Muller Ltd.; Homecrafts (Tas.) P/L; Jacoby, Mitchell & Co. P/L; T. H. Martin P/L.

TASMANIA

NORTH-WESTERN ZONE

The Annual Hamfest took place at Campbelltown on Sunday, 22nd November. The weather was ideal for the occasion, and the previous two days had been most unpleasant but this morning dawned fine and clear and developed into a perfect hot summer's day.

I tagged along with Ray TZ8RS and we managed to get to the 22nd Nov. 100-mile trip from Devonport passed quickly, with a bit of mobile QSO'ing with George TXL and his family in the west, and were ahead of us and travelling on a different route.

On arrival at the camp site we introduced ourselves at the H.Q. tent and were then issued with a map of the local area, and call signs printed on them—everyone then knew who was who, and it saved a lot of embarrassment later when some old bush name you couldn't place suddenly accented you unexpectedly!!

The prize-taking session was devoted to the 30 m. tx hunt. Everyone taking part was given a sealed envelope and told to drive towards Campbelltown and congregate at the road junction. We did just that, and on opening the envelopes and piecing together the clues someone finally came across the vital "missing link" which, with our items of interest which everyone had to collect or have in his possession—these included a soldering iron, W.I.A. badge, numerous coins such as pennies, shillings, also a mobile log sheet and such things as a bottle top, beer can, pine cone, a feather and a cigarette packet of a certain brand.

Ray and I were fortunate enough to come across the beer can, bottle top and pine cone; later we found a dead bird along the roadside, and although it had been in a state of rigor mortis for about 15 months (judging by the smell), the feathers were most valuable—this did a swap for a coin in exchange for one of our reserve stock of feathers, but not having a soldering iron or W.I.A. badge with us we made our way back to the camp site thinking we might have a fair chance as we had collected all the other items. However, Ray's swap was dashed as Len TKL had already "clocked in" 100% and so took out top honours.

What show have you got against a bloke who carries his soldering iron in his hip pocket—faithfully wears his W.I.A. badge and religiously keeps a mobile log—even before he had entered the contest!!

FOR SALE

Communications Transceiver, National NCX-3, 80-10 Mc, L.S.B.-U.S.B., full 500 Kc. coverage each band, hand, 10 m. crystals, 300 W. pep input, £425, O.N.O.

NCX-4 Power Supply also available if required.

Communications Receiver, National NC100-X, general coverage 540 Kc. to 30 Mc. Amateur and International Broadcast bandspread, a.m.-f.m., £190, O.N.O. (work, 45-643) (business); 45-3002 (private), Vic.

Stockists of Radio and Electronic

Components for the Amateur Constructor and Hobbyist

First Ring, Write or Call on

WILLIAM WILLIS & Co. Pty. Ltd.

428 Elizabeth St., Melb'ne. Ph. 34-6539

COMPUTER CIRCUIT BOARDS

containing transistors, resistors, condensers, diodes, etc., 2/- per transistor. We also stock 180V/0.75A diodes (two for 30/-) and 250V transistors (100V/15A, 47/- ea.).

AUSTRALIAN ELECTRONICS

(formerly "Electronics Associates")

76 View Street, Hobart, Tasmania.

Repairs to Receivers, Transmitters, constructing and testing; xtal conv., any frequency; Q5-ers, R9-ers, and transistorised equipment.

ECCESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 86-3777

Anyway, we in the N.W. had the consolation of winning the wooden spoon with George TXL arriving last himself!

Lunchtime saw small groups either grilling steaks or munching sandwiches. Amongst the N.W. Zone contingent I noticed Snow TKH, Ken TKL, Sid TZJ, Bruce KCL, Bob Wilson and Winston Nichols from Burnie; also Brian Ayres, Ian Killings, Robin -7, George TXL and family, and TDX, Ray and myself from Devonport. Quite a good roll-up.

Now at this stage my clever piece of detective work came into play—I noticed (unseen) Ken TKL chase around in the long grass and pounce on a couple of grasshoppers, like a four-year-old boy would, to place his victims in a tin, look furtively to the right and left, then proceed with red and real towards the creek; minutes later Ken returned with a couple of rice-cricket trout—about that!!

Further—I noticed (again unseen) Ray TZ8RS and Bob Wilson don adversarial and armed with pickaxes proceed towards the hills—most suspicious!! On following them I found both hard at work fossicking around amongst the rocks muttering "agale," "petrified wood," etc., etc. . . . Anybody yet got any clues as to who they were looking for?

The afternoon saw a rolling-pin throwing contest for XVYL, was again by Den TDK's XVYL noticed that the thrummed reel was into the air and entertaining the kids like a real Santa Claus.

The contest for guessing the resonant frequency of the h.f. tuned circuit intrigued quite a few. George TXL was the first to have a go—after many minutes of deliberation he finally gave a figure of 4.9 Mc. Everyone knowing how "cluey" George is, plotted their "guesses" around that figure. Ted TEJ was nearest with 4.9 Mc. George was pretty close himself. The V.H.F. Section was won by Winston Nichols, so the N.W. Zone notched up a victory.

A general meeting held in the open for all and sundry to air their grievances produced some lively debating; such items as a.m. versus s.w.b., pep power input, wet or dry for next year's Hamfest (no further comment), were all discussed. The thrummed reel was reached a pitch with a lively dog fight which developed, and which was eventually brought under control. All is well that ends well. So cheers for those who made it this year at Campbelltown that sums it up.

A Happy New Year to all. T.S. David TMS.

HAMADS

Minimum 5/-, for thirty words.

Extra words, 2d. each.

Advertisements under this heading will be accepted only from Amateurs and S.W.s. The Publishers reserve the right to reject any advertising which, in their opinion, is of a commercial nature. Copy must be received at P.O. Box 38, East Melbourne, C.S. Vic., by 10.30 a.m. and must be accompanied by the advertisement.

COLLINS KWM2 all band a.s.b

Transceiver, as new condition, complete with Collins FM2 solid state a.c. power supply and Collins mike, £500. S. G. McLean, VK5ME, 76-1491.

FOR SALE: Geloze 222TR, 6-band,

a.m./c.w. Transceiver, perfect, "as new" condition, complete with circuit, manual, etc. Cost £120, sell for £65. VK4JL, P.O. Box 30, Goondwindi (phone 684).

FOR SALE: T.C.A. Transceiver, 12v.,

d.c., converted to 146 Mc. f.m. net, complete with crystals (Channel B), car cradle and antenna, unit in working order, receiver needs alignment, £20. Command Receiver, 8-9 Mc., working, £5. Also have 240v. a.c. Power Supply and 12v. d.c. Supply for the above Command Rx. Nuvisior Converter for 2 metres, full working order, £10. Home-brew G.D.O. with power supply, £5. Philips Mantel Radio, 5 valve, new, £10. All inquiries answered. Reply P.O. Box 206, Liverpool, N.S.W.

FOR SALE: Wagner Model A1 Mobile, 5-band, 60 watt, s.s.b. Transceiver. Phone Horsham 2-2288, write or call C/o R. H. Leskie, T.V. Service, off Darlot St., Horsham, Vic.

FOR SALE:

13 tube, double conversion Communications Receiver, 160 to 10 metres, crystal filter, product detector, audio a.g.c., etc., £40. Table-top Transmitter, 160, 80 and 40 metres, module construction, complete with crystals, v.f.o., microphone and power supplies, £25. Ferguson Tape Recorder, as new, complete with several tapes and microphone, £25. Lot 59, Orchard Street, Glen Waverley, Vic., or 232-9492.

FOR SALE:

33 ft. Oregon Mast, selected timber, requires no guying, painted white, £5. Joystick Antenna with a.t.u., new, £5. Kyoritsu a.w.r. Meter, 52 or 75 ohms, £5. BM3 crystal Mike, with stand and p.t.t. switch, modified, £2/10/-, L. Hobbin, VK3VH, 24 Marshall Av., N. Clayton (near Monash Uni.), Vic.

GALAXY V, as new, complete with

home-built power supply, £250. R. Longworth, 6 Savoy Av., Killara, Sydney, N.S.W.

OSCILLOSCOPE for sale: R.T.V. &

H. 3-inch C.R.O., £12. Hard time-base; excellent horizontal and vertical amplifiers. Needs new tube, VCR139A, otherwise Al order. A. D. Proudfoot, 5 Andrew St., Horsham, Vic., VK3ADA.

SELL: Comm. Rx HQ170A, v.h.f., all

bands, 2 M. thru 160 M., all modes, inbuilt 2 and 6 M. convts., new. S. Widgery, 181 Victoria St., Ballarat.

SELL: Geloze G222 Transmitter, al-

tered for relay control, £65. Geloze G209 Receiver, £95. Both units in good condition. H. T. Swanton, VK4AUS, 16 Karma Avenue, East Malvern, Vic. Phone 211-3716.

SELL: Radio and Hobbies, 1943-1961,

Electronics World, 1959-1961. Popular Electronics and Electronics Illustrated, 1959-64, average price 4/-, prefer sell yearly lots or swap or buy parts for Delatheat Radio and Hobbies, October, 1964. C. MacKinnon, 173 Stewart St., Bathurst, N.S.W.

SELL: 100 and 500 Kc. Xtals, few left,

cheap, \$5.80. Also some power supplies units. A1, VK4SS, or ph. 46526 before 4 p.m. (Please add postage.)

TRANSMITTER for sale: AT14A,

pair 813's modulated by 811A's using Woden UM3 mod. trans., provision for extracting 120w. audio, modulation h.t. of 750, 1,000, 1,500v. for powering v.f.o., etc., rlg. £35 or offer. P. v. proofed Transmitter, 150w. Geloze v.f.o. driving QB3/300, £25 or offer. W. J. Bell, VK3WK, Wangoom, Tel. Grasmere 225.

WANTED: Beam Direction Indicator,

endless pot, aircraft tank, float unit. S. Widgery, 181 Victoria St., Ballarat.

A LARGE RANGE OF TRANSMITTERS, RECEIVERS, TEST GEAR, AND DISPOSALS RADIO PARTS AVAILABLE

★ SCR522 V.H.F. TRANSCEIVERS

Frequency range: 100-156 Mc., xtal locked. Completed with valves, less xtals. Brand new new condition. £13 plus freight.

★ METERS, P25 TYPE

0-500 uA., 52/6; 0.100 uA., £3/9/6; 0-1 mA., 45/-; 0-10 mA., 45/-; 0-50 mA., 45/-. Full range of Meters and Multi-Testers available.

★ CO-AXIAL CABLE

UR70 72 ohms, 3/16 inch diam., in 27-yard rolls, £1 plus 7/6 pack and post. In as new condition.

★ COLLINS MODULATION TRANSFORMERS

20 watts, 6,000 ohms p.p. primary, 6,000 ohms secondary. 35/- plus freight.

★ FIVE-INCH C.R.O.

Nagard Model 103, d.c. 10 Mc., 100 mV/CM sensitivity, fully calibrated time base, complete with power supply, £65.

★ PHILIPS TA155 C.R.O.

2 inch c.r.o. tube, £17 plus freight.

★ 80-40 METRE TRANSCEIVER

San Electronics QTR7. Tx: 6BQ5 p.a., 6BQ5 modulator, xtal locked. Rx: Tunes 3.5 to 11 Mc., 1 watt audio output, 230v. a.c., £45.

★ SAL39 AMPLIFIER KLYSTRONS

Pulse Service: 120w. input, 30kw. output, duty cycle 1%, freq. range 960-1230 Mc. C.w. Service: 50w. input approx., 300w. output approx. Ideal tube for 1296 Mc. band. £10 plus freight.

WANTED TO BUY

Communication Receivers, Test Equipment, etc. Call, write or phone. Equipment inspected and picked up at your convenience any night or week-end.

★ MINIATURE CAPACITORS

New shipment. 600 v.w. Values: 0.001, 0.02, 0.005, 0.0005, 0.0002, 0.0001 uF. £1 for 80 plus freight.

★ RESISTORS

1/4 watt, I.R.C., Welwyn, Eire, Ducon, Philips, £1 per 100.

★ CRYSTALS

Personal shoppers only, 10/- each.

★ RELAYS

P.M.G. 3000 type, 500 ohms and 500 ohms d.p.d.t., 7/6 each or 3 for £1.

★ SIGNAL GENERATORS

Type LSG10, 120 Kc. to 260 Mc., £13. Type LSG11, 120 Kc. to 390 Mc., provision for xtal, £15, both plus freight.

★ SPECIALS

813 Beam Tetrodes, 50/- each.

7-pin skirted Valve Sockets, P.T.F.E., insulation, silver plated, only 2/- each, c/w. shield.

★ POWER SUPPLIES

300v. at 150 mA., 6.3v. at 3 amp., fully enclosed, on 19-inch panel, £3, complete with meter £4.

★ C.R.O. TUBES

CV407, 10/- each; CV392, 10/- each.

★ TRANSISTORS

Brand new. OC72, OC44, 2N132, OC66, OC45, 8/- each. AT1139 Power Transistor, 30w., Class B, 30/-. Also Diodes: OA70, OA81, OA95, 3/6 each.

ANY QUERIES

Beginners are welcome, ask Jim and Laurie Gardiner any questions. They are Amateur Radio operators and will be only too pleased to assist.

ALL ITEMS FREIGHT EXTRA

UNITED TRADE SALES PTY. LTD.

280 LONSDALE ST., MELBOURNE, VIC. (Opp. Myers)


Phone 32-3815

2.5 Watts Output with 4dB Gain at 1000 Mc/s as a Tripler

TD-60

RCA-2N4012 "overlay" Transistor FREQUENCY MULTIPLICATION WITH POWER GAIN

at UHF and Microwave Frequencies

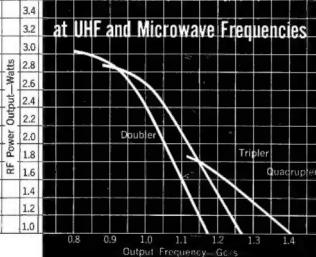

Input Power = 1 Watt

$V_C = 28$ Volts

Case Temp. (T_C) = 25° C.

Now for the first time, you can achieve frequency multiplication with power gain at microwave frequencies with a single solid-state device, the new 2N4012 silicon transistor. With this new "overlay" unit, you can greatly simplify circuit design as well as reduce costs. At 1 Gc/s, one single 2N4012 can replace both the transistor power amplifier and varactor diode stages previously required.

Offering frequency multiplication with power gain in the 1 Gc/s region, the 2N4012 as a doubler, tripler, and even as a quadrupler, extends transistor performance into the microwave region with watts of power! When used in a common-emitter configuration, this transistor provides stable operation—power output varies smoothly with changes in power input.

Find out how the 2N4012 can help you cut costs by eliminating the varactor and reduce the size of hardware in space, military, and commercial applications. For technical data, price, and delivery, contact Amalgamated Wireless Valve Co. Pty. Ltd., 348 Victoria Road, Rydalmere, N.S.W., or any interstate office.

	2N4012 DOUBLER	2N4012 TRIPLER
Output Power	3 (typ) 2.5 (min) Watts	
Output Frequency	800	1032 Mc/s
Input Frequency	400	336 Mc/s
Conversion Gain	4.8 (typ)	4 (min) dB
MAXIMUM RATINGS	V_{CBO} 65 Volts	
	V_{CEO} 40 Volts	
	V_{CEV} 65 Volts	
	V_{ESD} 4 Volts	
	I_C 1.5 Amperes	



AMALGAMATED WIRELESS VALVE CO. PTY. LTD.
SYDNEY • MELBOURNE • BRISBANE • ADELAIDE • PERTH • HOBART